# LMZ22003,LMZ22005,LMZ23603,LMZ23605

Application Note 2085 LMZ23605/03, LMZ22005/03 Evaluation Board



Literature Number: SNVA457A

## LMZ23605/03, LMZ22005/03 Evaluation Board

### National Semiconductor Application Note 2085 Alan Martin March 27, 2011



### Introduction

The LMZ23605/03, LMZ22005/03 evaluation boards are designed to be an easy-to-use platform to evaluate the full capabilities of this family of SIMPLE SWITCHER® power modules. The PCB construction has excellent thermal performance and includes extra locations for optional components that may not be required in the end application.

The LMZ23605/03 can accept an input voltage rail between 6V and 36V and the LMZ22005/03 can accept an input voltage rail between 6V and 20V. The devices can deliver an adjustable and highly accurate output voltage as low as 0.8V and as high as 6V. The control architecture is constant frequency PWM with emulated current mode sensing. The control loop operates well with low ESR output capacitors such as ceramics or specialty polymer. The precision enable input allows for programmable UVLO on the input supply or flexibility in sequencing. The external soft-start capacitor facilitates controlled output rise time at startup. The module family is a reliable and robust solution with cycle-by-cycle valley current limit to protect for over current or short-circuit faults. Additionally there is thermal shutdown protection, and they will start up into a pre-biased output. The free-running switching frequency is 812 kHz (typ) and a 650 kHz to 950 kHz synchronization range is supported.

## **Board Specifications**

- V<sub>IN</sub> = 6V to 36V (LMZ22005/03 limited to 20V)
- Enable UVLO = 5.7V
- V<sub>OUT</sub> = 3.3V
- I<sub>OUT</sub> = 0 to 5A (LMZ23603 and LMZ22003 limited to 3A)
- $\theta_{JA} = 12^{\circ}C / W, \ \theta_{JC} = 1.9^{\circ}C/W$
- PCB designed on four layers; Inner are 2 oz; Outer are 3 oz.
- Measures 3.5 in. x 3.5 in. (8.9 cm x 8.9 cm) and is 62mil (.062") thick of FR4 laminate material
- Max ambient temp of 70°C at full 5A load (12 Vin)

For additional circuit considerations refer to the Applications Section of the LMZ23605/03 or LMZ22005/03 data sheets. For negative output voltage connections follow the method shown in AN-2027.



FIGURE 1. Evaluation Board Simplified Schematic

## **Performance Characteristics**

### LMZ23605 3.3Vout Efficiency @ 25°C Ambient









LMZ23605 Load and Line Regulation @ 25°C Ambient







LMZ23605 3.3Vout Dissipation @ 85°C













30131618



# AN-2085

### **Notes**

Solder turrets are located on the edge of the PCB assembly for evaluation hookup to bench test equipment. The Enable input turret is designed for direct connection to the  $V_{IN}$  turret. There is a resistive divider implemented on the board that establishes the 5.5V precision UVLO level of the board. A common user change to this divider is to raise the value of  $R_{ENT}$  to increase the operating UVLO to that of the target application. Refer to the respective data sheet for calculation. Note that if in the end application the module pin 3 enable voltage does not exceed 5.5V at maximum Vin, then enable clamp zener D1 can be omitted.

Each implementation of the evaluation board is preset to 3.3V output; with current rating and maximum input voltage rating dictated by the model of module installed. A common user change is to adjust the output voltage for different requirements. A table of suggested resistor pairs are listed in Figure 1 for quick reference.

Locations are provide for testing the operation as a coincident turn-on tracking supply (slave). To implement this feature, remove  $C_{\rm SS}$  and install Rtkt and Rtkb. Calculations are suggested in the respective data sheets.

A turret is also provided for applying a clock to synchronize the module switching frequency anywhere between 650 kHz and 950 kHz. Note that a sustained "logic one" on this input corresponds to "zero hertz" and will cause the module to stop switching.

J1 and J2 are for input and output noise measurement. To implement this feature, populate the 1uF blocking capacitors and the 49.9 ohm source resistors. Install Amphenol coax connectors type 112404 (Digikey #ACX1051).The added R-C network forms a 2X scope probe when used in conjunction with an input termination of 50 ohms at the oscilloscope, providing 5 times more sensitivity than a conventional 10x probe.

J3 is for connection to a frequency response analyzer such as A/P Instruments (Ridley) or Venable Industries products. Refer to the FRA operating manual for this connection. Note: Do not place any type of shorting jumper to these three posts as that will cause a malfunction.

Inductor current can be monitored by connecting a loop of between module pin 7 (Vout) and the Co array. First cut the top side conducting etch between the two vias adjacent to pin 7, then install a 5" loop of 22 ga insulated wire in the two vias. Monitor the inductor sense loop with an AC/DC oscilloscope current probe.

The Vin input plane has solder mask openings where an input LC network can be placed to accommodate improved differential mode and conducted EMI performance.

Additional component mounting pads are available to experiment with alternative Cin and Cout combinations. See Figure 6 for corresponding schematic locations.

## PCB View and layout diagrams

Gerber and CAD files can be downloaded from the LMZ23605 /03, LMZ22005/03 respective product folders.



FIGURE 2. Top View of Assembly

C 2011 NSC GND GND Simple Switcher© Power Module Evaluation Board LMZ23605 36V 5A LMZ23603 36V 3A LMZ22005 20V 5A LMZ22003 20V 3A U1 Τ2 Co5 Cos Cin Ci පේ 7 0 D۵  $\cap$ Rent Sync Rtk Rfra Rtkb O GND 50 J3 EN Cin5 VTrk Vin O  $\bigcirc$ (O) Vo ٦ (O) O GND ٦ 0000 30131609

FIGURE 3. Top Layer



www.national.com







FIGURE 7. LMZ2360x / LMZ2200x PCB CAD package schematic DNP = Component not populated

TABLE 1. Bill of Materials, $V_{IN} = 6V$ to 36V, $V_{OUT} = 3.3V$ , $I_{OUT (MAX)} = 5A$ (3A)
Note: The same BOM applies to all implementations

Designator	Description	Case Size	Manufacturer	Manufacturer P/N	Quantity
U1	SIMPLE SWITCHER®	TO-PMOD-7	National Semiconductor	LMZ23605TZ or LMZ23603TZ or LMZ22005TZ or LMZ22003TZ	1
C <sub>IN</sub> 1 C <sub>IN</sub> 5 C <sub>O</sub> 1 C <sub>O</sub> 6	0.047 µF, X7R, 50V	1206	Yageo America	CC1206KRX7R9BB473	4
C <sub>IN</sub> 2 C <sub>IN</sub> 3	10 µF, X5R, 50V	1210	Taiyo Yuden	UMK325BJ106MM-T	2
C <sub>IN</sub> 6 OPT	150 μF,Aluminum Electrolytic, 50V	G	Panasonic	EEE-FK1H151P	1
C <sub>O</sub> 2 OPT	100 µF, X5R, 6.3V	1210	TDK	C3225X5R0J107M	1
C <sub>O</sub> 5	220 μF, Specialty Polymer, 6.3V		Panasonic	EEF-UE0J221LR	1
C <sub>FF</sub>	DNP				
C <sub>SS</sub>	0.47µF, X7R, 16V	0805	AVX	0805YC474KAT2A	1
D1	5.1V 200mW	SOD-323	Diodes Inc.	MMSZ5231BS-7-F	1
R <sub>ENB</sub>	12.7 kΩ	0805	Panasonic	ERJ-6ENF1272V	1
R <sub>ENT</sub>	42.2 kΩ	0805	Panasonic	ERJ-6ENF4222V	1
R <sub>ENH</sub>	100 Ω	0805	Vishay-Dale	CRCW0805100RFKEA	1
R <sub>FBT</sub>	3.32 kΩ	0805	Vishay-Dale	CRCW08053K32FKEA	1
R <sub>FBB</sub>	1.07 kΩ	0805	Vishay-Dale	CRCW08051K07FKEA	1
R <sub>FRA</sub>	23.7 Ω	0805	Vishay-Dale	CRCW080523R7FKEA	1
R <sub>FF</sub>	DNP				
R <sub>SN</sub>	1.50 kΩ	0805	Vishay-Dale	CRCW08051K50FKEA	1

# Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at: www.national.com

Products		Design Support	
Amplifiers	www.national.com/amplifiers	WEBENCH® Tools	www.national.com/webench
Audio	www.national.com/audio	App Notes	www.national.com/appnotes
Clock and Timing	www.national.com/timing	Reference Designs	www.national.com/refdesigns
Data Converters	www.national.com/adc	Samples	www.national.com/samples
Interface	www.national.com/interface	Eval Boards	www.national.com/evalboards
LVDS	www.national.com/lvds	Packaging	www.national.com/packaging
Power Management	www.national.com/power	Green Compliance	www.national.com/quality/green
Switching Regulators	www.national.com/switchers	Distributors	www.national.com/contacts
LDOs	www.national.com/ldo	Quality and Reliability	www.national.com/quality
LED Lighting	www.national.com/led	Feedback/Support	www.national.com/feedback
Voltage References	www.national.com/vref	Design Made Easy	www.national.com/easy
PowerWise® Solutions	www.national.com/powerwise	Applications & Markets	www.national.com/solutions
Serial Digital Interface (SDI)	www.national.com/sdi	Mil/Aero	www.national.com/milaero
Temperature Sensors	www.national.com/tempsensors	SolarMagic™	www.national.com/solarmagic
PLL/VCO	www.national.com/wireless	PowerWise® Design University	www.national.com/training

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

### LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

### Copyright© 2010 National Semiconductor Corporation

For the most current product information visit us at www.national.com



National Semiconductor Americas Technical Support Center Email: support@nsc.com Tel: 1-800-272-9959

National Semiconductor Europe Technical Support Center Email: europe.support@nsc.com National Semiconductor Asia Pacific Technical Support Center Email: ap.support@nsc.com National Semiconductor Japan Technical Support Center Email: jpn.feedback@nsc.com

### **IMPORTANT NOTICE**

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Audio	www.ti.com/audio	Communications and Telecom	www.ti.com/communications
Amplifiers	amplifier.ti.com	Computers and Peripherals	www.ti.com/computers
Data Converters	dataconverter.ti.com	Consumer Electronics	www.ti.com/consumer-apps
DLP® Products	www.dlp.com	Energy and Lighting	www.ti.com/energy
DSP	dsp.ti.com	Industrial	www.ti.com/industrial
Clocks and Timers	www.ti.com/clocks	Medical	www.ti.com/medical
Interface	interface.ti.com	Security	www.ti.com/security
Logic	logic.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense
Power Mgmt	power.ti.com	Transportation and Automotive	www.ti.com/automotive
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video
RFID	www.ti-rfid.com		
OMAP Mobile Processors	www.ti.com/omap		
Wireless Connectivity	www.ti.com/wirelessconnectivity		

**TI E2E Community Home Page** 

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2011, Texas Instruments Incorporated