

# LM3414HV

*Application Note 2076 LM3414HV 1A 65V LED Driver Evaluation Board*



Literature Number: SNVA451B

# LM3414HV 1A 65V LED Driver Evaluation Board

National Semiconductor  
Application Note 2076  
SH Wong  
August 10, 2010



## Introduction

The LM3414HV is a 65V floating buck LED driver that designed to drive up to 18 pieces of serial High Brightness LEDs (HBLEDs) with up to 1000mA LED forward current. With the incorporation of the proprietary Pulse-Level-Modulation (PLM) technology, the LM3414HV requires no external current sensing resistor to facilitate LED current regulation. The LM3414HV features a dimming control input (DIM pin) that allows PWM dimming control. The LM3414HV is available in LLP-8 (3mm x 3mm outline) and ePSOP8 to fulfil the requirements of small solution size and high thermal performance respectively. In order to demonstrate the performance of the LM3414 family, the LM3414HV is selected for the evaluation boards because of the wide input voltage range (4.5V to 65V) providing the best flexibility to fit the requirements of different applications. Two versions of evaluation board with identical schematic are available with the LM3414HV in either LLP-8 or PSOP-8 package. The board with LLP-8 package demonstrates the high power density of the device. The board with PSOP-8 package demonstrates the functionality of the LM3414HV with enhanced thermal performance. The schematic, bill of materials and PCB layout for the evaluation boards are provided in this document. The evaluation boards can be adapted to different application requirements by changing the values of a few components only. This evaluation board is also suitable for the LM3414 with maximum acceptable input voltage reduced to 42VDC.


## Standard Settings of the LM3414HV Evaluation Board

Vin range: 4.5V to 65V

No. of LEDs: 1 - 18

LED current: 1A


Switching frequency: 500 kHz

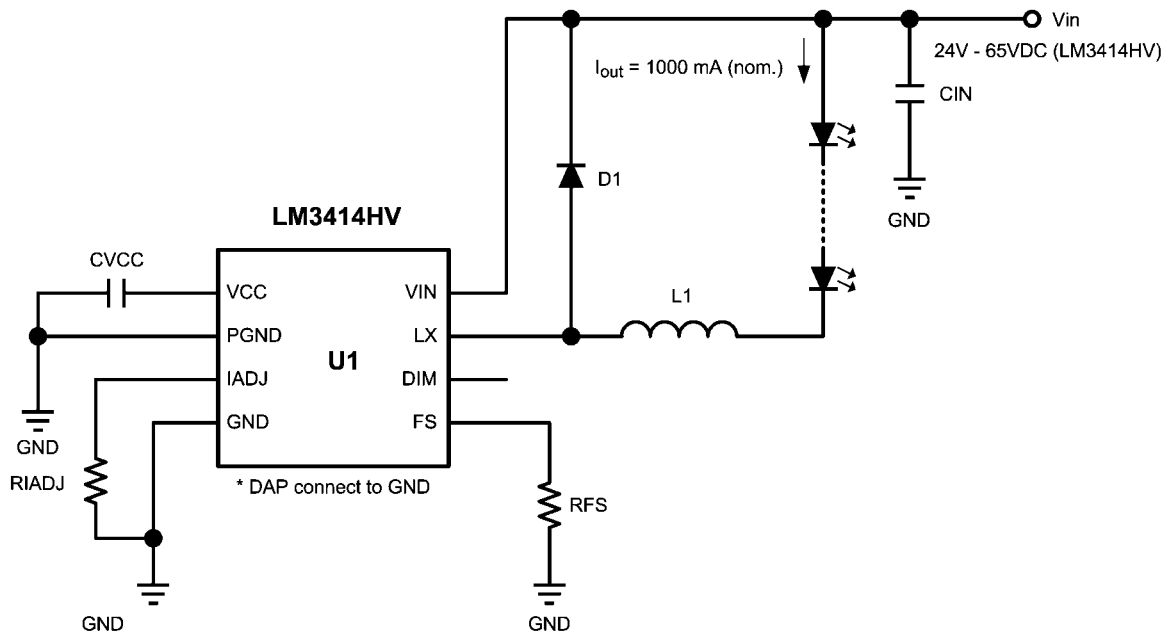

30128701

FIGURE 1. Standard Schematic for the LM3414HV Evaluation Board

## Board Connectors and Test Pins

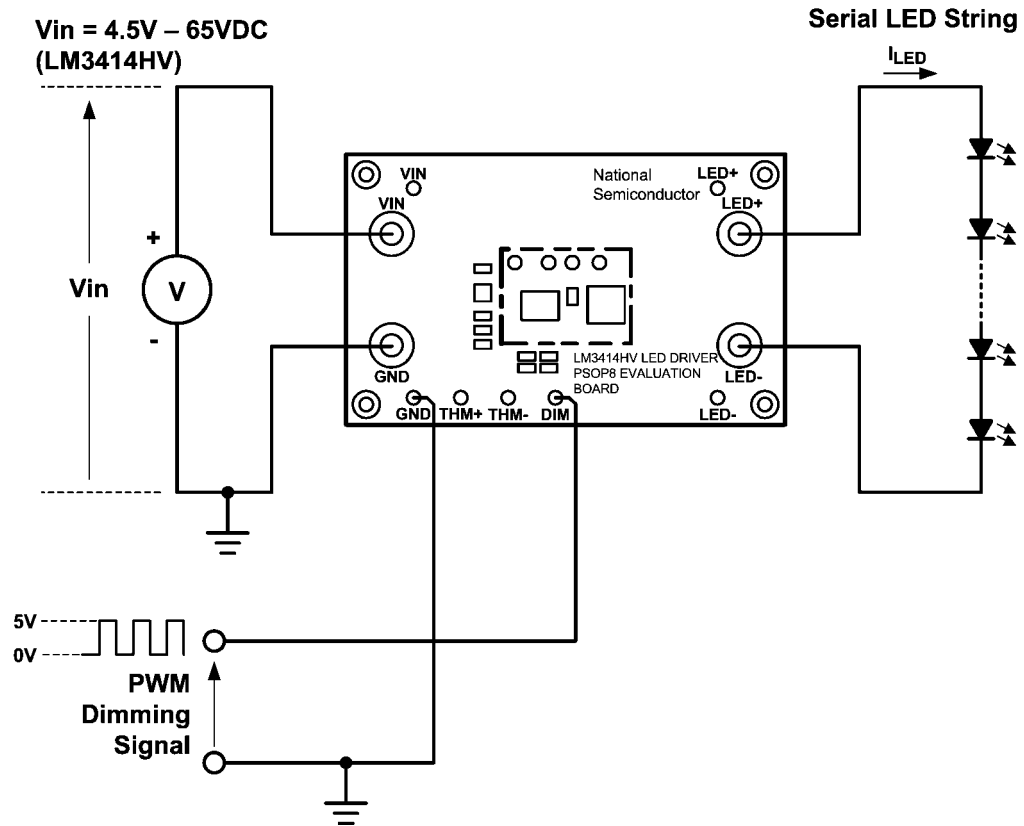

30128702

FIGURE 2. Connection Diagram

Terminal Designation	Description
VIN	Power supply positive (+ve) connection
GND	Power supply negative (-ve) connection
LED+	Connect to cathode of the serial LED string
LED-	Connect to anode of the serial LED string
DIM	PWM dimming signal input (TTL signal compatible)
THM+	Connect to PTC thermal sensor for thermal foldback control
THM-	Connect to PTC thermal sensor for thermal foldback control

## Connecting to LEDs and Power Supply

The LM3414HV evaluation board can be powered by a DC voltage source in the range of 4.5V to 65V through the banana-plug type connectors (VIN and GND) on the board as shown in figure 2. This evaluation board is designed to provide 1A ( $I_{LED}$ ) output current to a LED string containing up to 18 pieces of serial HBLEDs. The anode and cathode of the LED string should connect to the LED+ and LED- banana-plug type connectors on the board respectively. By default, the LM3414HV on the evaluation board is enabled. The LEDs will light up as long as appropriate input voltage is applied to the evaluation board.

## Adjusting the Output Current

The resistor RIADJ defines the output current of the LM3414HV evaluation board. The default value of RIADJ is 3.09k $\Omega$ , which sets the LED driving current to 1A. The LED current can be changed by adjusting the value of RIADJ with equation (1):

$$I_{LED} = \frac{3125 \times 10^3}{R_{IADJ}} \text{ mA} \quad (1)$$

Table 1 shows the suggested value of RIADJ for common output current settings:

$I_{LED}$ (mA)	$R_{IADJ}$ (k $\Omega$ )
350	8.93
400	7.81
500	6.25
600	5.21
700	4.46
800	3.91
900	3.47
1000	3.13

TABLE 1. Examples for RIADJ Setting

## Adjusting the Switching Frequency

The resistor RFS defines the switching frequency of the LM3414HV evaluation board. The default value of the RIADJ is 40k $\Omega$  that sets the switching frequency to 500kHz. The LED current is adjustable by altering the resistance of RFS according to the equation (2):

$$f_{SW} = \frac{20 \times 10^6}{R_{FS}} \text{ kHz} \quad (2)$$

Table 2 shows the suggested value of RFS for different switching frequencies:

$f_{SW}$ (kHz)	$R_{FS}$ (k $\Omega$ )
250	8.93
500	7.81
1000	6.25

TABLE 2. Examples for RFS Setting

When setting the switching frequency, it is necessary to ensure the on time of the inductor switch is no shorter than

400ns; otherwise the driving current to the LEDs will increase and may eventually damage the LEDs.

## Design Example

Assuming a LED string containing six serial HBLEDs is being driven by the board with 700mA ( $I_{LED}$ ). The forward voltages of one HBLED with 700mA driving current under different operation temperatures are:

$$V_{f(60C)} @ 700\text{mA} = 3.0\text{V}$$

$$V_{f(25C)} @ 700\text{mA} = 3.2\text{V}$$

$$V_{f(-10C)} @ 700\text{mA} = 3.5\text{V}$$

### Step 1. Defining input voltage range

Because the LM3414HV is a floating buck LED driver, the input voltage to the LED driver must be higher than the total forward voltage of the LEDs under all conditions. As the forward voltage of a common HBLED could increase as the driving current increases or the operation temperature decreases, it is essential to ensure the minimum supply voltage is at least 10% higher than the possible highest forward voltage of the LED string. For example, assuming the forward voltage of a HBLED is 3.2V at  $T_A = 25^\circ\text{C}$  and 3.5V at  $T_A = -10^\circ\text{C}$  at 700mA driving current. When 6 pieces of LED are connected in series, the total forward voltage of the LED string at  $25^\circ\text{C}$  and  $-10^\circ\text{C}$  are 19.2V and 21V respectively. In order to secure current regulation under  $-10^\circ\text{C}$ , the input voltage should not be lower than 23.1V. In this example, a standard 24V DC power supply with no more than  $\pm 3\%$  output voltage variation can be used.

### Step 2. Defining switching frequency $f_{SW}$

When the maximum LED forward voltage and minimum input voltage are identified, the switching frequency of the LM3414HV can be defined. The switching frequency of the LM3414HV must be set in the range of 250kHz to 1MHz. Because the LM3414HV is designed to operate in continuous conduction mode (CCM) with 400ns minimum switch ON time limit, the maximum allowable switching frequency is restricted by the minimum input voltage,  $V_{IN(MIN)}$  and maximum LED forward voltage,  $V_{f(MAX)}$  according to equation (3):

$$f_{SW} \leq \frac{V_{f(MIN)}}{V_{IN(MAX)} \times 400 \times 10^{-6}} \text{ kHz}$$

$$\text{where } 250 \text{ kHz} \leq f_{SW} \leq 1 \text{ MHz} \quad (3)$$

In this example, because a 24V DC power supply with  $\pm 3\%$  output voltage variation is used,  $V_{IN(MAX)}$  is 24.72V. The minimum forward voltage of the LED string  $V_{f(MIN)}$  is 18V because the forward voltage of the LED string will be at the lowest level when the operation temperature rises to  $60^\circ\text{C}$ . According to equation (3), with  $V_{IN(MAX)}=24.72\text{V}$  and  $V_{f(MIN)}=18\text{V}$ , the switching frequency,  $f_{SW}$  should not set higher than 1.82MHz. However, because the switching frequency of the LM3414HV must set in the range of 250kHz to 1MHz, 1MHz switching frequency is selected.

### Step 3. Inductor Selection

The inductance of the inductor, L1 can be decided according to the switching frequency and output current settings determined in step 1 and step 2. The inductance must be adequate to maintain the LM3414HV to operate in CCM. The minimum inductance can be calculated by following equation (4):

$$L \geq \frac{(V_{IN(MAX)} - V_{f(MIN)}) \times V_{f(MIN)} \times 10^6}{I_{LED} \times V_{IN(MAX)} \times f_{SW} \times K} \mu\text{H}$$

$$\text{where } K = \frac{I_{RIP(P-P)}}{I_{LED}} \quad \left| \quad 0 < K < 1.8 \right. \quad (4)$$

In equation (4),  $I_{LED}$  is the average output current of the LM3414HV circuit to drive the LED string.  $I_{RIP(P-P)}$  is the peak-to-peak value of the inductor current ripple. Assuming that the required LED current is 700mA, 50% inductor current ripple and 1MHz switching frequency, the inductance should be no less than 14uH. Because common power inductor carries +/-20% inductance tolerance, a standard 18uH inductor with +/-20% tolerance can be used.

Other than deciding a suitable inductance value, it is essential to ensure the peak inductor current is not exceeding the rated saturation current of the inductor. The peak inductor current is governed by the following equation:

$$I_{L(PEAK)} = \left[ \frac{(V_{IN(MAX)} - V_{f(MIN)}) \times V_{f(MIN)}}{L_{(MIN)} \times V_{IN(MAX)} \times f_{SW} \times 2} + I_{LED} \right] \text{A} \quad (5)$$

In equation (5),  $I_{L(PEAK)}$  is the peak inductor current. As a 18uH with +/- 20% variation is used, the minimum inductance  $L_{(MIN)}$  is 14.4uH. With 700mA LED current, the peak inductor current is 836mA, thus a standard 18uH power inductor with 1A saturation current ( $I_{SAT}$ ) can be used.

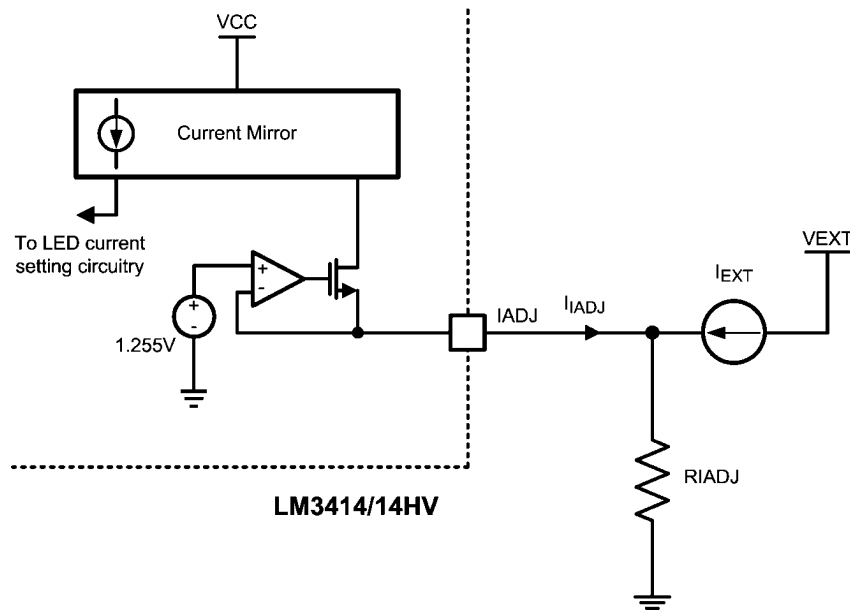


FIGURE 3. Reducing LED current with external current to the IADJ pin

$$I_{LED} = \left[ \left( \frac{1.255}{R_{IADJ}} - I_{EXT} \right) \times 2490 \times 10^3 \right] \text{mA} \quad (7)$$

In equation (7),  $I_{EXT}$  is the external current being injected into RIADJ. As  $I_{EXT}$  increases,  $I_{LED}$  decreases.

Figure 4 shows a practical thermal foldback control circuit which reduces the LED current when the temperature of the LED string is exceeding certain preset threshold. Because the temperature threshold for thermal foldback control depends

## PWM Dimming Control

The average LED current can be controlled by applying PWM dimming signal across the DIM and GND terminals of the LM3414HV evaluation board. The board accepts standard TTL level dimming signal. The output of the board is enabled when the DIM terminal is pulled high. The average LED current is adjustable according to the ON duty ratio of the PWM dimming signal by equation (6):

$$I_{LED(Avg)} = D_{DIM} \times \left( \frac{3125 \times 10^3}{R_{IADJ}} \right) \text{mA} \quad (6)$$

In equation (6),  $I_{LED(AVG)}$  is the average current flows through the LED string and  $D_{DIM}$  is the ON duty ratio of the PWM dimming signal being applied to the DIM pin of the LM3414HV.

## Analog Dimming Control

As the output current of the LM3414HV is defined by the current being drawn to GND through RIADJ proportionally, analog dimming control (true output current control) can be accommodated by applying external current to RIADJ of the LM3414HV evaluation board. Figure 3 shows an example circuit for analog dimming control. With analog dimming control. Injecting additional current through the RIADJ to GND can effectively reduce the LED current ( $I_{LED}$ ). The relationship of  $I_{LED}$  and  $I_{EXT}$  is governed by equation (7).

on end application, the components required in this thermal foldback control circuitry are not included in the LM3414HV evaluation board. Physical pads and connections for R1, R2 and Q1 have been reserved on the board for component mounting. In order to detect the temperature of the LED string, a Positive Temperature Coefficient (PTC) thermistor, RPTC should be connected across the THM+ and THM- terminals of the LM3414HV evaluation board. In figure 4, the bipolar transistor, Q1 is biased by a potential divider composed of R1 and RPTC. When the temperature of the LEDs rises, the volt-

age drop across RPTC increases as the resistance of RPTC increases. As the emitter voltage of Q1 reaches 1.255V, thermal foldback control is activated and the LED current reduces according to  $I_{EXT}$ .

mal foldback control is activated and the LED current reduces according to  $I_{EXT}$ .

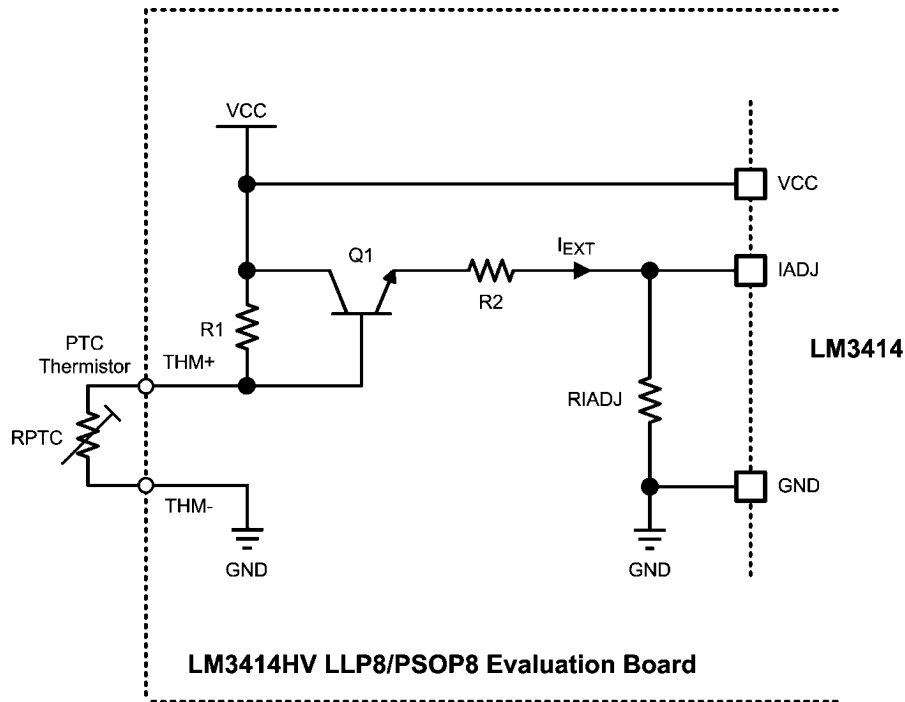


FIGURE 4. Thermal Foldback Control with PTC thermistor

### Design Example

The LM3414HV evaluation board is used to drive a LED string at 700mA and thermal foldback control is needed to take place when the temperature of the LED strings exceeds 80°C as presented in Figure 5.

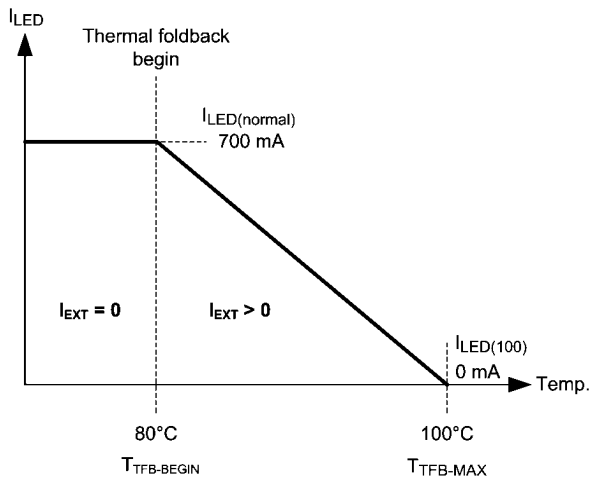


FIGURE 5. Reduction of LED current with thermal foldback control

Assume the resistance of the PTC thermistor under 25°C, 80°C and 100°C are:

- $R_{PTC(25C)} = 330\Omega$
- $R_{PTC(80C)} = 1.2k\Omega$
- $R_{PTC(100C)} = 10k\Omega$

In Figure 5, the LED current with the LED temperature below 80°C ( $I_{LED(normal)}$ ) is 700mA. As the temperature of the LED goes up to 80°C, thermal foldback begins and reduces the LED driving current with respect to the increase of resistance of RPTC. As the temperature of the LEDs reaches 100°C, the LED current reduces to zero. Provided that the resistance of the thermistor RPTC under 80°C and 100°C are 1.2kΩ and 10kΩ respectively, the values of R1 and R2 can be calculated following the steps listed below.

At 80°C:

$$\begin{aligned} \therefore I_{R2} &= 0A \\ \therefore V_E &= V_{IADJ} = 1.255V \\ V_{PTC} &= V_E + V_{BE} \\ &= 1.255V + 0.7V \\ &= 1.955V \\ V_{PTC} &= V_{CC} \times \frac{R_{PTC(80^\circ C)}}{R1 + R_{PTC(80^\circ C)}} \\ &= 5.4V \times \frac{1.2 k\Omega}{R1 + 1.2 k\Omega} \end{aligned}$$

$$R1 = 11.08 k\Omega \tag{8}$$

At 100°C:

$$\therefore I_{LED} = 0A$$

$$\therefore I_{EXT} = \frac{1.255V}{RIADJ} = 281 \mu A$$

$$= \frac{1}{R2} \times \left[ \frac{V_{CC} \times R_{PTC(100^\circ C)}}{R1 + R_{PTC(100^\circ C)}} - (V_{BE} + V_{IADJ}) \right] A$$


$$= \frac{1}{R2} \times \left[ \frac{5.4V \times 10 \text{ k}\Omega}{11.06 \text{ k}\Omega + 10 \text{ k}\Omega} - (0.7V + 1.255V) \right] A$$

$$R_2 = 2.17 \text{ k}\Omega$$

(9)

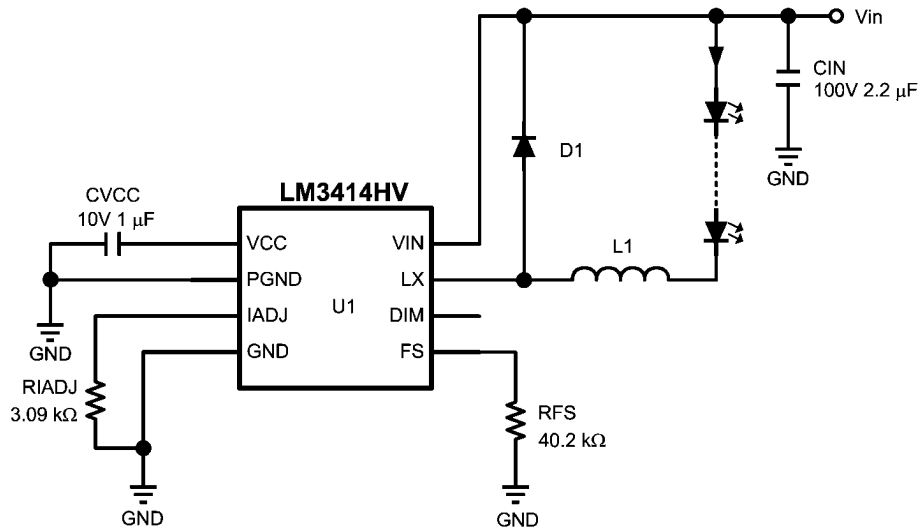
### Tiny Board Outline

The tiny packages of the LM3414 family are exceptionally suitable for the applications that require high output power in limited space. In order to demonstrate the high power density of the LM3414HV, the core circuitry of this evaluation boards are completed in compact form factors: 22mm x 19mm for LLP-8 package, 26mm x 19mm for PSOP-8 package. The schematic of the core circuitry is as shown in Figure 6. The core circuitry can be extracted by cutting out from the PCB frame of the board as shown in Figure 7.




30128725

FIGURE 6. Core Circuitry of the LM3414HV Evaluation Boards

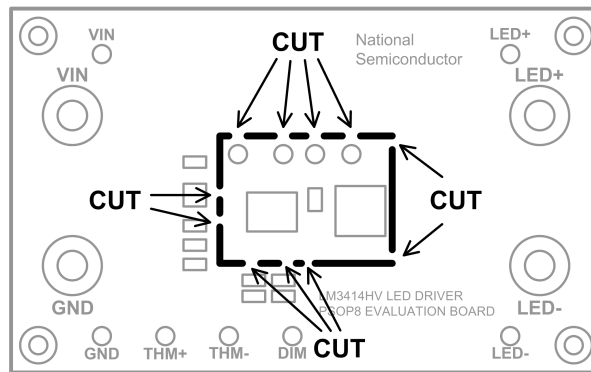

30128726

FIGURE 7. Extracting the core circuitry from the LM3414HV evaluation boards

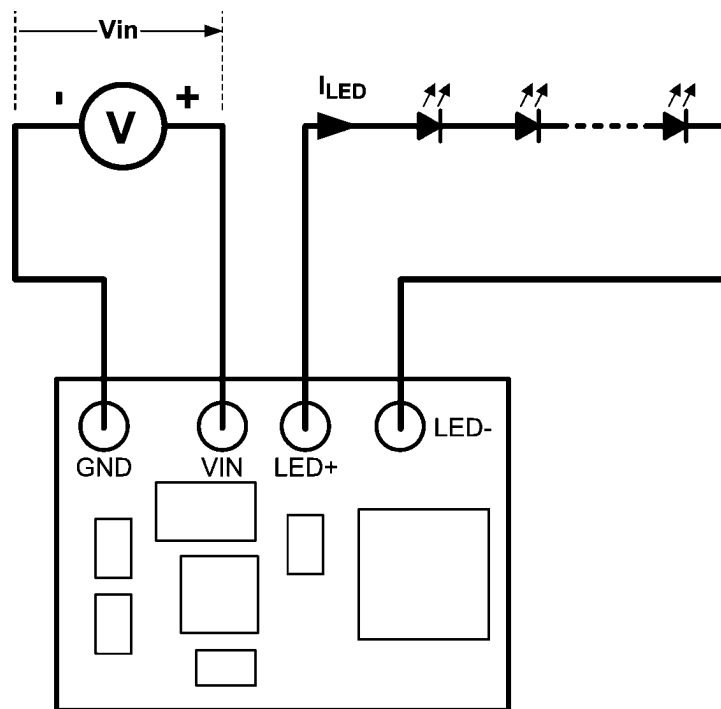

30128727

**FIGURE 8. Connecting to the core circuitry**

The board of the core circuitry features four connection pads for connections to DC power supply and LED string, as shown in Figure 8. To ensure thermal performance of the board, a heatsink attaches to the bottom layer of the board may be required depending on actual operation environment.


## Bill of Materials

Designation	Description	Package	Manufacturer Part #	Vendor
U1	LED Driver IC, LM3414HV	LLP8 / PSOP8	LM3414MH	NSC
D1	Schottky Diode 100V 2A		SS2PH10-M3/84A	Vishay
L1	Power Inductor 47 $\mu$ H		MMD-08EZ-470M-S1	MAG.Layers
CIN	Cap MLCC 100V 2.2 $\mu$ F X7R 1210	1210	GRM32ER72A225KA35L	Murata
CVCC	Cap MLCC 10V 1 $\mu$ F X5R 0603	603	GRM185R61A105KE36D	Murata
RIADJ	Chip Resistor 3.09 k $\Omega$ 1% 0603	603	CRCW06033K09FKEA	Vishay
RFS	Chip Resistor 40.2 k $\Omega$ 1% 0603	603	CRCW060340K2FKEA	Vishay
VIN, GND, LED+, LED-	Banana Jack 5.3(mm) Dia	5.3 (mm) Dia.	575-8	KEYSTONE
VIN, GND, LED+,LED-, THM+, THM-, DIM,	Turret 2.35(mm) Dia	2.35 (mm) Dia.	1502-2	KEYSTONE
PCB	LM3414EVAL PCB 85 X 54 (mm)	85 X 54 (mm)		NSC
Q1	NPN Bipolar Transistor	SOT23		
R1,R2,RFS_1, RFS_2,RIADJ_1	NA	603		
JP1,JP2,JP3	NA	603		



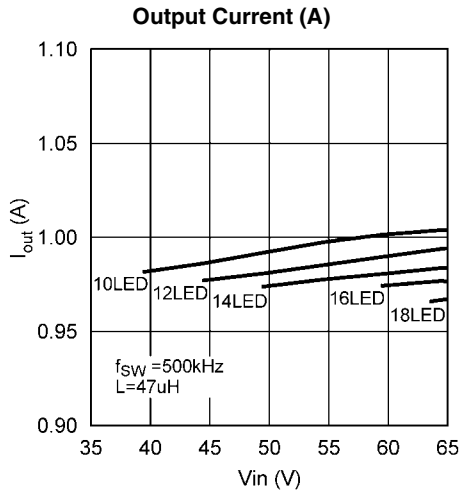
## Typical Performance Characteristics


All curves taken at  $V_{IN} = 48V$  with configuration in typical application for driving twelve power LEDs with four output channels active and output current per channel = 350 mA.  $T_A = 25^\circ C$ , unless otherwise specified.




30128730

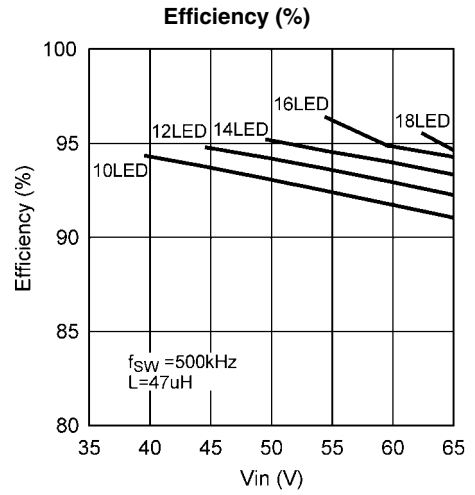


30128731

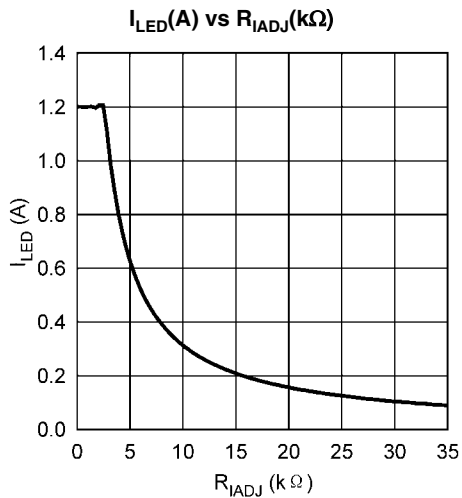


30128732

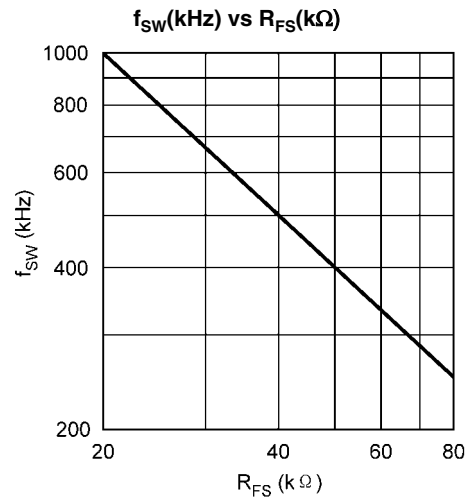

30128733

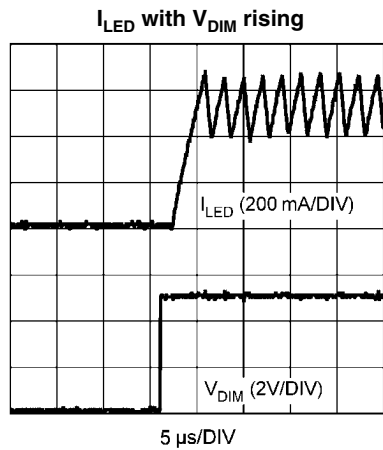


30128708

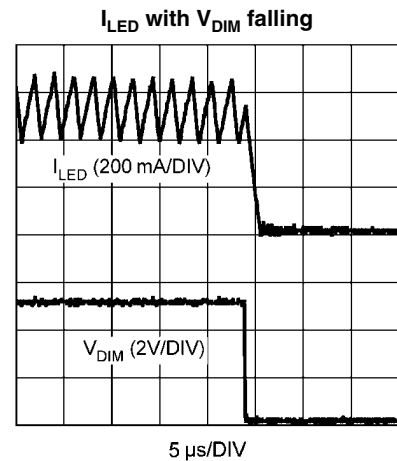


30128709
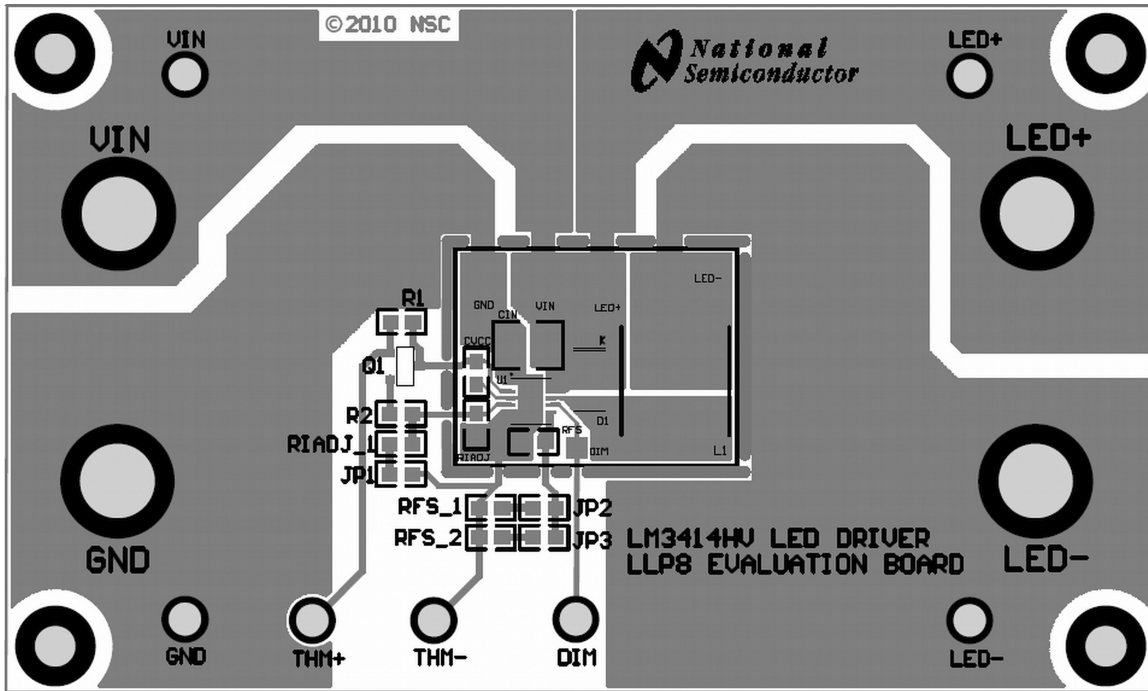
# Evaluation Board Layout (LLP-8 Package)



Top Layer and Top Overlay


30128712

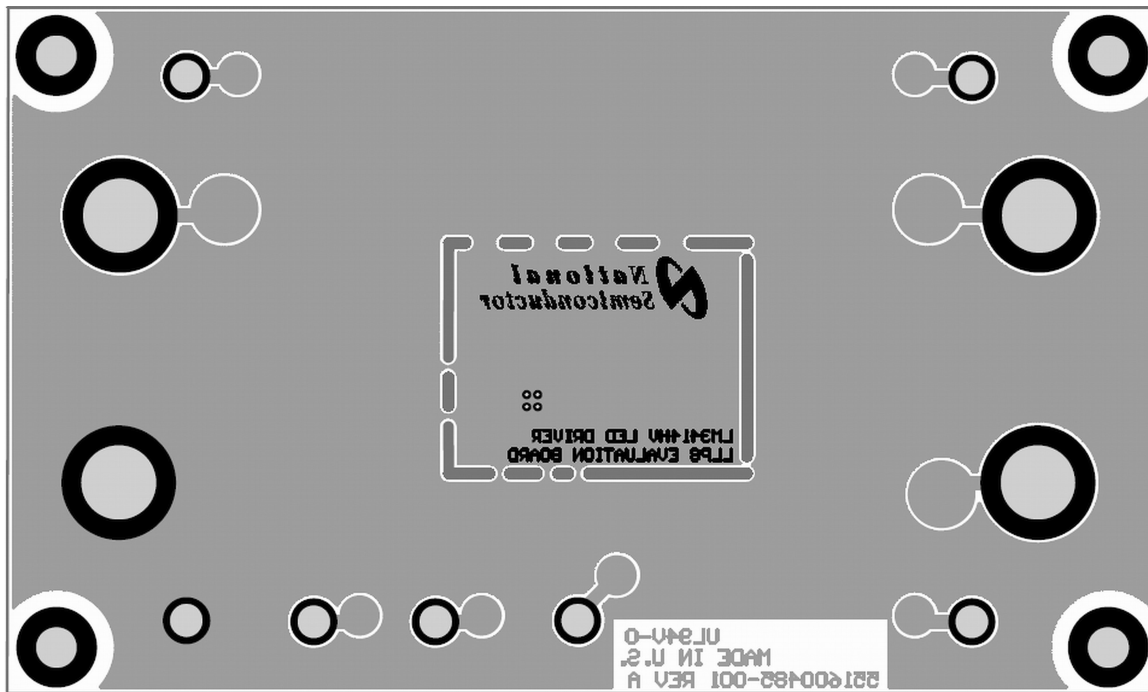

Bottom Layer and Bottom Overlay


30128713
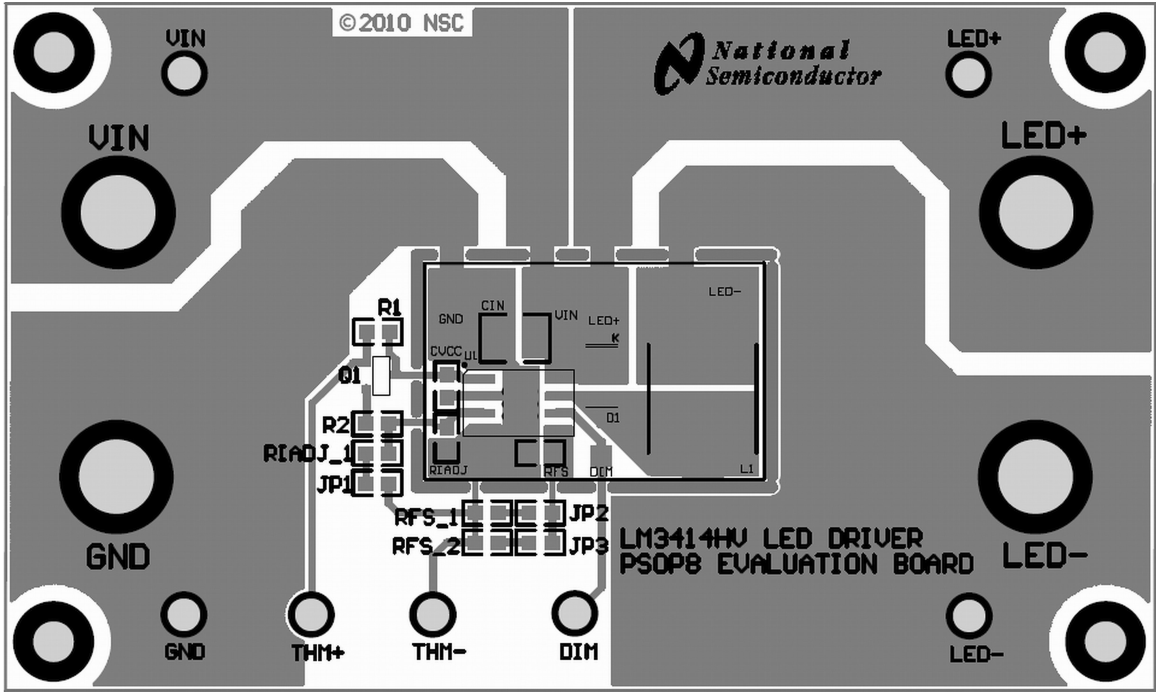
# Evaluation Board Layout (PSOP-8 Package)



Top Layer and Top Overlay

30128714

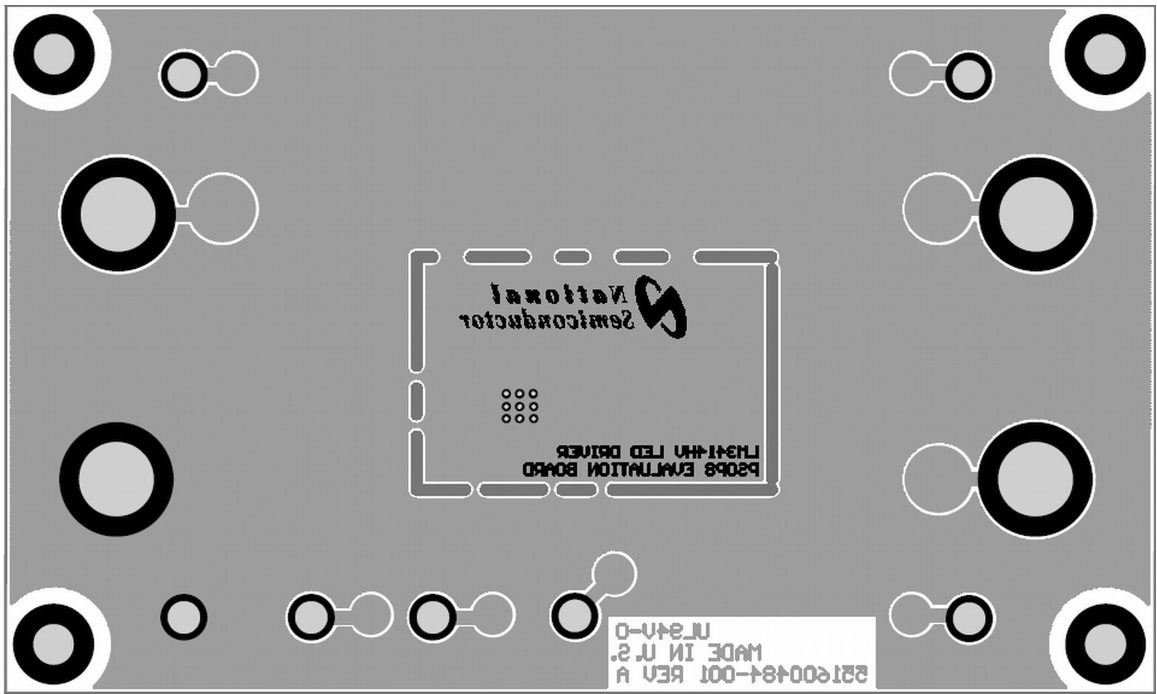

Bottom Layer and Bottom Overlay

30128715

# Notes

AN-2076

## Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:  
[www.national.com](http://www.national.com)

Products		Design Support	
Amplifiers	<a href="http://www.national.com/amplifiers">www.national.com/amplifiers</a>	WEBENCH® Tools	<a href="http://www.national.com/webench">www.national.com/webench</a>
Audio	<a href="http://www.national.com/audio">www.national.com/audio</a>	App Notes	<a href="http://www.national.com/appnotes">www.national.com/appnotes</a>
Clock and Timing	<a href="http://www.national.com/timing">www.national.com/timing</a>	Reference Designs	<a href="http://www.national.com/refdesigns">www.national.com/refdesigns</a>
Data Converters	<a href="http://www.national.com/adc">www.national.com/adc</a>	Samples	<a href="http://www.national.com/samples">www.national.com/samples</a>
Interface	<a href="http://www.national.com/interface">www.national.com/interface</a>	Eval Boards	<a href="http://www.national.com/evalboards">www.national.com/evalboards</a>
LVDS	<a href="http://www.national.com/lvds">www.national.com/lvds</a>	Packaging	<a href="http://www.national.com/packaging">www.national.com/packaging</a>
Power Management	<a href="http://www.national.com/power">www.national.com/power</a>	Green Compliance	<a href="http://www.national.com/quality/green">www.national.com/quality/green</a>
Switching Regulators	<a href="http://www.national.com/switchers">www.national.com/switchers</a>	Distributors	<a href="http://www.national.com/contacts">www.national.com/contacts</a>
LDOs	<a href="http://www.national.com/ldo">www.national.com/ldo</a>	Quality and Reliability	<a href="http://www.national.com/quality">www.national.com/quality</a>
LED Lighting	<a href="http://www.national.com/led">www.national.com/led</a>	Feedback/Support	<a href="http://www.national.com/feedback">www.national.com/feedback</a>
Voltage References	<a href="http://www.national.com/vref">www.national.com/vref</a>	Design Made Easy	<a href="http://www.national.com/easy">www.national.com/easy</a>
PowerWise® Solutions	<a href="http://www.national.com/powerwise">www.national.com/powerwise</a>	Applications & Markets	<a href="http://www.national.com/solutions">www.national.com/solutions</a>
Serial Digital Interface (SDI)	<a href="http://www.national.com/sdi">www.national.com/sdi</a>	Mil/Aero	<a href="http://www.national.com/milaero">www.national.com/milaero</a>
Temperature Sensors	<a href="http://www.national.com/tempensors">www.national.com/tempensors</a>	SolarMagic™	<a href="http://www.national.com/solarmagic">www.national.com/solarmagic</a>
PLL/VCO	<a href="http://www.national.com/wireless">www.national.com/wireless</a>	PowerWise® Design University	<a href="http://www.national.com/training">www.national.com/training</a>

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

#### LIFE SUPPORT POLICY

**NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION.** As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2010 National Semiconductor Corporation

For the most current product information visit us at [www.national.com](http://www.national.com)



**National Semiconductor**  
Americas Technical  
Support Center  
Email: [support@nsc.com](mailto:support@nsc.com)  
Tel: 1-800-272-9959

**National Semiconductor Europe**  
Technical Support Center  
Email: [europe.support@nsc.com](mailto:europe.support@nsc.com)

**National Semiconductor Asia**  
Pacific Technical Support Center  
Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

**National Semiconductor Japan**  
Technical Support Center  
Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated