

LM5035

Application Note 1435 LM5035 Evaluation Board



Literature Number: SNVA143

LM5035 Evaluation Board

National Semiconductor
Application Note 1435
Steve Schulte
January 2006



Introduction

The LM5035 evaluation board is designed to provide the design engineer with a fully functional power converter based on the Half Bridge topology to evaluate the LM5035 controller. The evaluation board is provided in an industry standard quarter-brick footprint.

The performance of the evaluation board is as follows:

- Input operating range: 36V to 75V
- Output voltage: 3.3V
- Output current: 0 to 30A
- Measured efficiency: 89% at 30A, 92% at 15A
- Frequency of operation: 400kHz
- Board size: 2.28 x 1.45 x 0.5 inches
- Load Regulation: 0.2%
- Line Regulation: 0.1%
- Line UVLO (33.9V/31.9V on/off)
- Line OVP (79.4V/78.3V off/on)
- Hiccup current limit

The printed circuit board consists of 6 layers; 2 ounce copper outer layers and 3 ounce copper inner layers on FR4 material with a total thickness of 0.062 inches. The unit is designed for continuous operation at rated load at 40°C and a minimum airflow of 200 CFM.

Theory of Operation

Power converters based on the Half Bridge topology offer high efficiency and good power handling capability in applications up to 500 Watts. The operation of the transformer causes the flux to swing in both directions, thereby better utilizing the magnetic core.

The Half Bridge converter is derived from the Buck topology family, employing separate high voltage (HO) and low voltage (LO) modulating power switches with independent pulse width timing. The main difference between the topologies are, the Half Bridge topology employs a transformer to provide input / output ground isolation and a step down or step up function.


Each cycle, the main primary switch turns on and applies one-half the input voltage across the primary winding, which has 8 turns. The transformer secondary has 2 turns, leading to a 4:1 step-down of the input voltage. For an output voltage of 3.3V the composite duty cycle (D) of the primary switches varies from approximately 75% (low line) to 35% (high line).

The secondary employs synchronous rectification controlled by the LM5035. During soft-start, the sync FET body diodes act as the secondary rectifiers until the main transformer energizes the gate drivers. The DLY resistor programs the non-overlap timing for the sync FETs to maximize efficiency while eliminating shoot through current.

Feedback from the output is processed by an amplifier and reference, generating an error voltage, which is coupled back to the primary side control through an optocoupler. The COMP input to the LM5035 greatly increases the achievable loop bandwidth. The capacitance effect (and associated pole) of the optocoupler is reduced by holding the voltage across the optocoupler constant. The LM5035 voltage mode controller pulse width modulates the error signal with a ramp signal derived from the line voltage (feedforwarding) to reduce the response time to input voltage changes. A standard "type III" network is used for the compensator.

The evaluation board can be synchronized to an external clock with a recommended frequency range of 420kHz to 500kHz.

Theory of Operation (Continued)

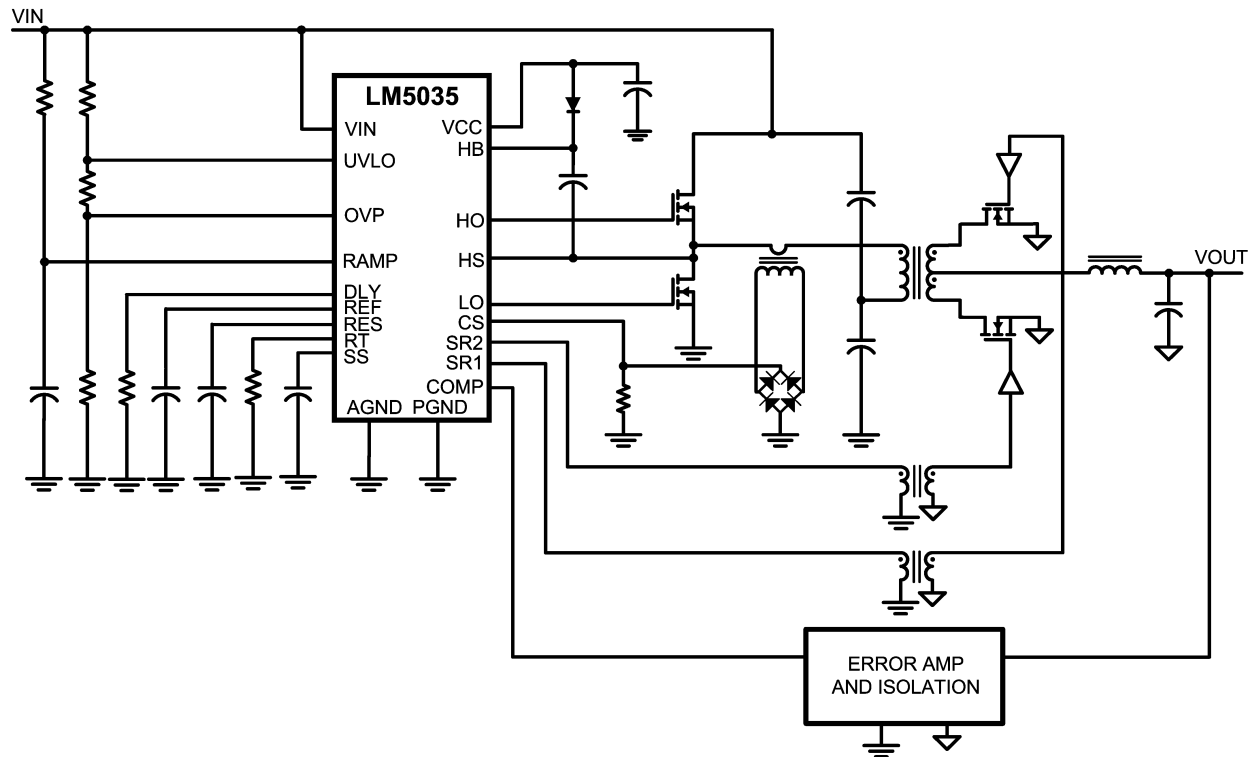

Simplified Half Bridge Converter

20177301

Powering and Loading Considerations

When applying power to the LM5035 evaluation board certain precautions need to be followed. A misconnection can damage the assembly.

Proper Connections

When operated at low input voltages the evaluation board can draw up to 3.5A of current at full load. The maximum rated output current is 30A. Be sure to choose the correct connector and wire size when attaching the source supply and the load. Monitor the current into and out of the evaluation board. Monitor the voltage directly at the output terminals of the evaluation board. The voltage drop across the load connecting wires will cause inaccurate measurements. This is especially true for accurate efficiency measurements.

Source Power

The evaluation board can be viewed as a constant power load. At low input line voltage (36V) the input current can reach 3.5A, while at high input line voltage (75V) the input current will be approximately 1.5A. Therefore, to fully test the LM5035 evaluation board a DC power supply capable of at least 85V and 5A is required.

The power supply must have adjustments for both voltage and current. The power supply and cabling must present low impedance to the evaluation board. Insufficient cabling or a high impedance power supply will cause voltage droop during turn-on due to the evaluation board inrush current. If large enough, this droop will cause a chattering condition

upon power up. This chattering condition is an interaction with the evaluation board undervoltage lockout, the cabling impedance and the inrush current.

Loading

An appropriate electronic load, with specified operation down to 1.0V minimum, is desirable. The resistance of a maximum load is 0.11Ω. The high output current requires thick cables! If resistor banks are used there are certain precautions to be taken. The wattage and current ratings must be adequate for a 30A, 100W supply. Monitor both current and voltage at all times. Ensure there is sufficient cooling provided for the load.

Air Flow

Full power loading should never be attempted without providing the specified 200 CFM of air flow over the evaluation board. A stand-alone fan should be provided.

Powering Up

Using the ON/OFF pin (J2) provided will allow powering up the source supply with the current level set low. It is suggested that the load be kept low during the first power up. Set the current limit of the source supply to provide about 1.5 times the wattage of the load. As you remove the connection from the ON/OFF pin to ground (J1), immediately check for 3.3 volts at the output.

A most common occurrence, that will prove unnerving, is when the current limit set on the source supply is insufficient for the load. The result is similar to having the high source


Powering Up (Continued)

impedance referred to earlier. The interaction of the source supply folding back and the evaluation board going into undervoltage shutdown will start an oscillation, or chatter, that may have undesirable consequences.

A quick efficiency check is the best way to confirm that everything is operating properly. If something is amiss you can be reasonably sure that it will affect the efficiency adversely. Few parameters can be incorrect in a switching power supply without creating losses and potentially damaging heat.

Over Current Protection

The evaluation board is configured with hiccup over-current protection. In the event of an output overload (approximately 35A) the unit will discharge the softstart capacitor, which disables the power stage. After a delay the softstart is released. The shutdown, delay and slow recharge time of the softstart capacitor protects the unit, especially during short circuit event where the stress is highest.

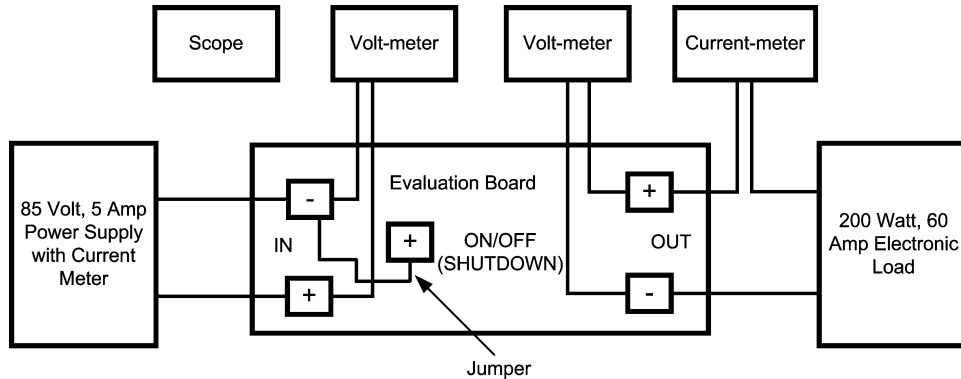

Typical Evaluation Setup

20177302


Performance Characteristics

TURN-ON WAVEFORMS

When applying power to the LM5035 evaluation board a certain sequence of events occurs. Soft-start capacitor values and other components allow for a minimal output voltage for a short time until the feedback loop can stabilize without overshoot. Figure 1 shows the output voltage during a typical start-up with a 48V input and a load of 5A. There is no overshoot during startup.

OUTPUT RIPPLE WAVEFORMS


Figure 2 shows the transient response for a load change from 15A to 22.5A. The upper trace shows minimal output voltage droop and overshoot during the sudden change in output current shown by the lower trace.

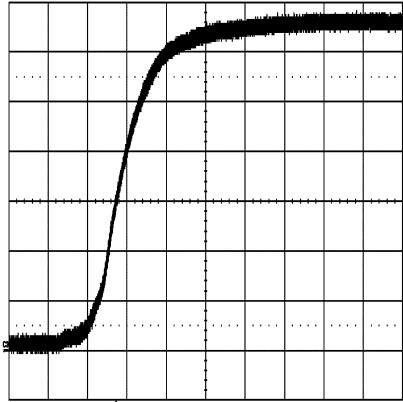

20177304

Conditions: Input Voltage = 48VDC
 Output Current = 5A
 Trace 1: Output Voltage Volts/div = 50mV
 Horizontal Resolution = 0.5ms/div


FIGURE 1.

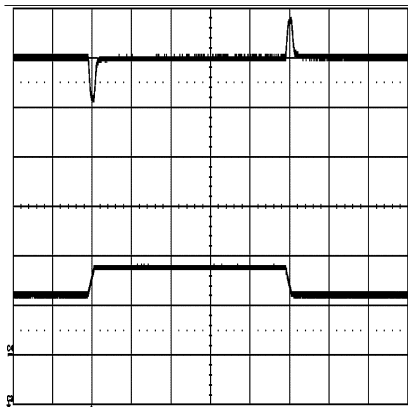

20177305

Conditions: Input Voltage = 48VDC
 Output Current = 15A to 22.5A
 Upper Trace: Output Voltage Volts/div = 50mV
 Lower Trace: Output Current = 15A to 22.5A to 15A
 Horizontal Resolution = 0.5ms/div

FIGURE 2.

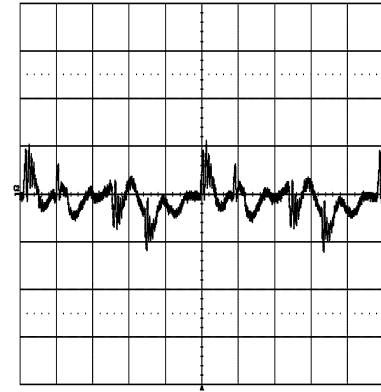

20177306


Conditions: Input Voltage = 48VDC
 Output Current = 30A
 Bandwidth Limit = 20MHz
 Trace 1: Output Ripple Voltage Volts/div = 20mV
 Horizontal Resolution = 1μs/div

FIGURE 3.

Figure 3 shows typical output ripple seen across the output terminals (with standard 10μF and 1μF ceramic capacitors) for an input voltage of 48V and a load of 30A. This waveform is typical of most loads and input voltages.

Figures 4 and 5 show the drain voltage of Q1 with a 5A load. Figure 4 represents an input voltage of 36V and Figure 5 represents an input voltage of 72V.

Figure 6 shows the gate voltages of the synchronous rectifiers. The deadtime provided by the 20kΩ DLY resistor is difficult to see at this timescale.

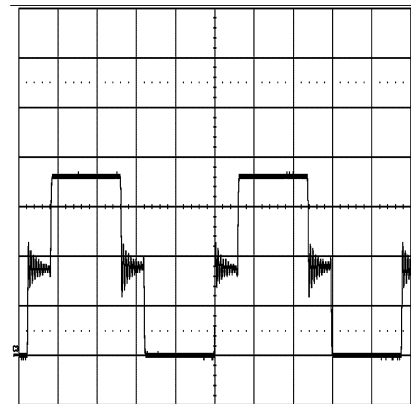


20177307

Conditions: Input Voltage = 36VDC
 Output Current = 5A
 Trace 1: Q1 drain voltage Volts/div = 10V
 Horizontal Resolution = 1μs/div

FIGURE 4.

Performance Characteristics


(Continued)

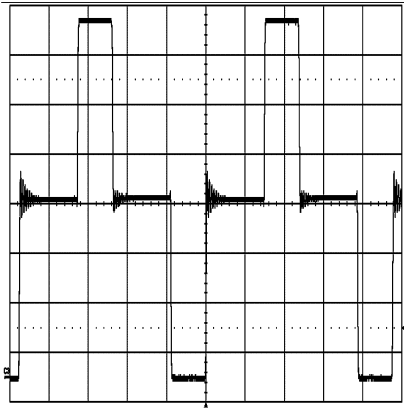

20177308

Conditions: Input Voltage = 72VDC
 Output Current = 5A
 Trace 1: Q2 drain voltage Volts/div = 10V
 Horizontal Resolution = 1 μ s/div

FIGURE 5.

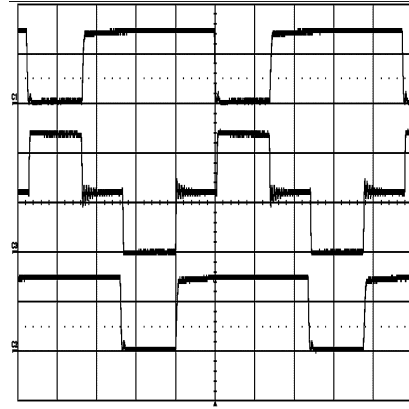


20177309

Conditions: Input Voltage = 48VDC
 Output Current = 5A
 Upper Trace: SR1, Q4 gate Volts/div = 5V
 Middle Trace: HS, Q2 drain Volts/div = 20V
 Lower Trace: SR2, Q6 gate Volts/div = 5V
 Horizontal Resolution = 1 μ s/div

FIGURE 6.

Application Circuit

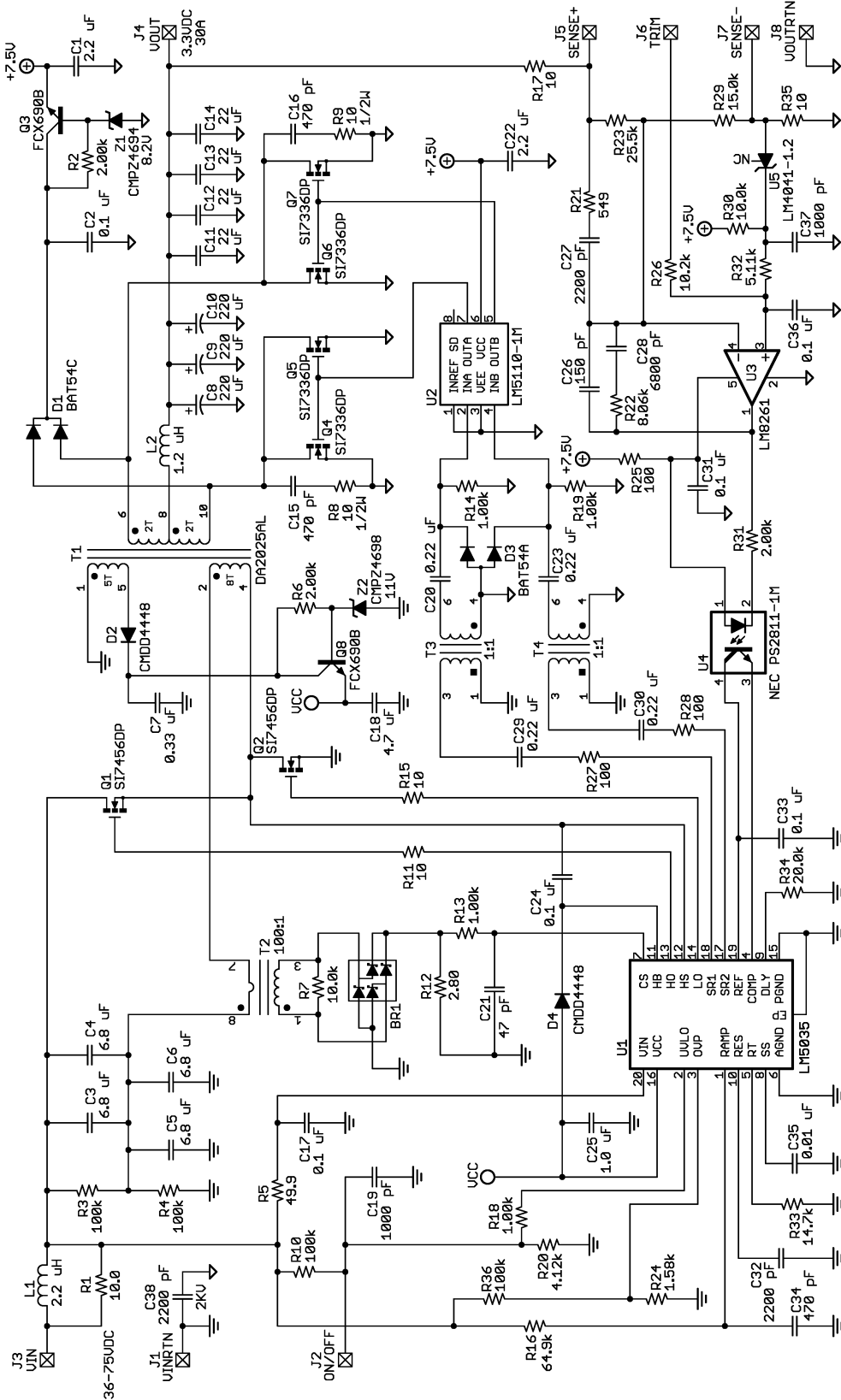


Application Circuit: Input 36 to 75V, Output 3.3V, 30A

20177318

DESIGNATOR	QTY	PART NUMBER	DESCRIPTION	VALUE
BR1	1	BAT54BRW	RECTIFIER, BRIDGE, DIODES INC	30V
C1,22	2	C2012X7R1C225K	CAPACITOR, 0805 X7R CER, TDK	2.2 μ , 16V
C2,31,33,36	4	C1608X7R1H104K	CAPACITOR, 0603 X7R CER, TDK	0.1 μ , 50V
C3 - 6	4	C4532X7R1H685M	CAPACITOR, 1812 X7R CER, TDK	6.8 μ , 50V
C7	1	C2012X7R1H334K	CAPACITOR, 0805 X7R CER, TDK	0.33 μ , 50V
C8 - 10	3	6TPE220MI	CAPACITOR, POSCAP, SANYO	220 μ , 6.3V
C11 - 14	4	C3216X5R0J226M	CAPACITOR, 1206 X5R CER, TDK	22 μ , 6.3V
C15, 16	2	C0805C471M5RAC	CAPACITOR, 0805 COG CER, KEMET	470p, 50V
C17, 24	2	C2012X7R2A104K	CAPACITOR, 0805 X7R CER, TDK	0.1 μ , 100V
C18	1	C3216X7R1C475K	CAPACITOR, 1206 X7R CER, TDK	4.7 μ , 16V
C19,37	2	C1608X7R1H102K	CAPACITOR, 0603 X7R CER, TDK	1000p, 50V
C20,23,29,30	4	C1608X7R1E224K	CAPACITOR, 0603 X7R CER, TDK	0.22 μ , 25V
C21	1	C1608C0G1H470J	CAPACITOR, 0603 X7R CER, TDK	47p, 50V
C25	1	C1608X7R1C105K	CAPACITOR, 0603 X7R CER, TDK	1.0 μ , 16V
C26	1	C1608C0G1H151J	CAPACITOR, 0603 COG CER, TDK	150p, 50V
C27,32	2	C1608C0G1H222J	CAPACITOR, 0603 COG CER, TDK	2200p, 50V
C28	1	C1608C0G 1H682J	CAPACITOR, 0603 COG CER, TDK	6800p, 50V
C35	1	C1608C0G 1E103J	CAPACITOR, 0603 COG CER, TDK	0.01 μ , 25V
C34	1	C1608C0G1H471J	CAPACITOR, 0603 COG CER, TDK	470p, 50V
C38	1	C4532X7R3D222K	CAPACITOR, 1812 X7R CER, TDK	2200p, 2000V
D1	1	BAT54C	DIODE, SOT-23 SCHOTTKY, VISHAY	200mA, 30V
D2,4	2	CMDD4448	DIODE, SOD-323, CENTRAL SEMI	250mA, 75V
D3	1	BAT54A	DIODE, SOT-23 SCHOTTKY, VISHAY	200mA, 30V
L1	1	RLF7030T-2R2M5R4	INDUCTOR, TDK	2.2 μ H, 5.4A
L2	1	SER2010-122MX	INDUCTOR, COILCRAFT	1.2 μ H, 37A
Q1,2	2	SI7456DP	N-FET, SILICONIX	100V, 25m Ω
Q3,8	2	FCX690B	NPN, ZETEX	45V, 2A
Q4 - 7	4	SI7336ADP	N-FET, SILICONIX	30V, 3m Ω
R1,11,15	3	CRCW080510R0F	RESISTOR, 0805, VISHAY	10
R7,30	2	CRCW06031002F	RESISTOR, 0603, VISHAY	10k Ω
R2	1	CRCW08052001F	RESISTOR, 0805, VISHAY	2.00k Ω
R3,4	2	CRCW06031003F	RESISTOR, 0603, VISHAY	100k Ω
R5	1	CRCW080549R9F	RESISTOR, 0805, VISHAY	49.9 Ω
R6	1	CRCW08051002F	RESISTOR, 0805, VISHAY	10k Ω
R8,9	2	CRCW201010R0F	RESISTOR, 2010, VISHAY	10 Ω
R10,36	2	CRCW08051003F	RESISTOR, 0805, VISHAY	100k Ω
R16	1	CRCW08056492F	RESISTOR, 0805, VISHAY	64.9k Ω
R12	1	CRCW06032R80F	RESISTOR, 0603, VISHAY	2.8 Ω
R13,14,18,19	4	CRCW06031001F	RESISTOR, 0603, VISHAY	1k Ω
R17,35	2	CRCW060310R0F	RESISTOR, 0603, VISHAY	10 Ω
R20	1	CRCW06034121F	RESISTOR, 0603, VISHAY	4.12k Ω
R21	1	CRCW06035490F	RESISTOR, 0603, VISHAY	549 Ω
R22	1	CRCW06038061F	RESISTOR, 0603, VISHAY	8.06k Ω
R23	1	CRCW06032552F	RESISTOR, 0603, VISHAY	25.5k Ω
R24	1	CRCW06031581F	RESISTOR, 0603, VISHAY	1.58k Ω
R25,27,28	3	CRCW06031000F	RESISTOR, 0603, VISHAY	100 Ω
R26	1	CRCW06031022F	RESISTOR, 0603, VISHAY	10.2k Ω
R29	1	CRCW06031502F	RESISTOR, 0603, VISHAY	15k Ω
R31	1	CRCW06032001F	RESISTOR, 0603, VISHAY	2.00k Ω
R32	1	CRCW06035111F	RESISTOR, 0603, VISHAY	5.11k Ω


DESIGNATOR	QTY	PART NUMBER	DESCRIPTION	VALUE
R33	1	CRCW06031472F	RESISTOR, 0603, VISHAY	14.7k Ω
R34	1	CRCW06032002F	RESISTOR, 0603, VISHAY	20k Ω
T1	1	DA2025-AL	POWER XFR, COILCRAFT	8:5:2:2
T2	1	P8208	CURRENT XFR, PULSE ENG	100:1, 10A
T3,4	2	SM76924	GATE XFR, DATATRONIC	1:1
U1	1	LM5035MH	CONTROLLER, NATIONAL SEMI	
U2	1	LM5110-1M	DRIVER, DUAL, NATIONAL SEMI	
U3	1	LM8261M5	OPAMP, SOT23-5, NATIONAL SEMI	
U4	1	PS2811-1M	OPTO-COUPLER, NEC	
U5	1	LM4041AIM3-1.2	REFERENCE, SOT23, NATIONAL SEMI	1.225V
Z1	1	CMPZ4694	ZENER, SOT23, CENTRAL SEMI	8.2V, 5%
Z2	1	CMPZ4698	ZENER, SOT23, CENTRAL SEMI	11V, 5%
J1,2,3,5,6,7	6	3104-2-00-01-00-00-08-0	0.040" PIN, MILL-MAX	
J4,8	2	3231-2-00-01-00-00-08-0	0.080" PIN, MILL-MAX	

PCB Layouts

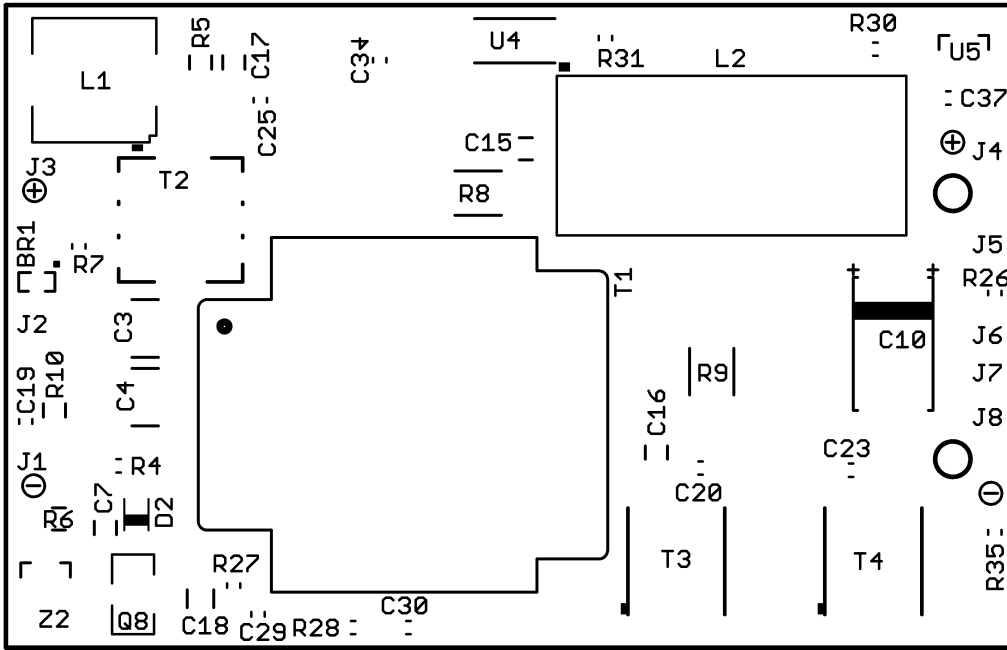

Top Side


20177310

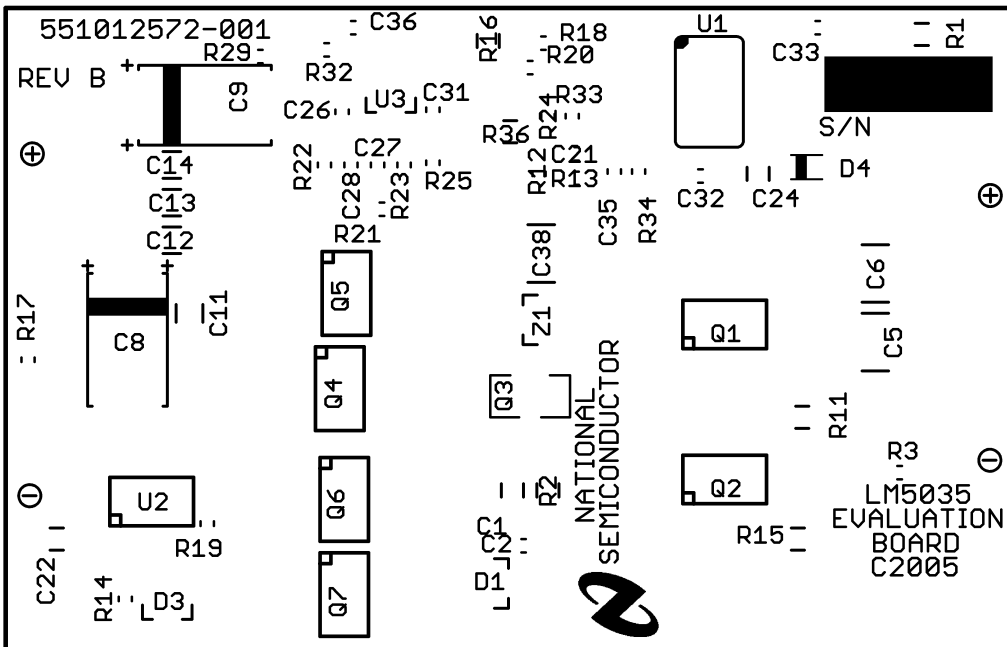

Bottom Side


20177311

PCB Layouts (Continued)

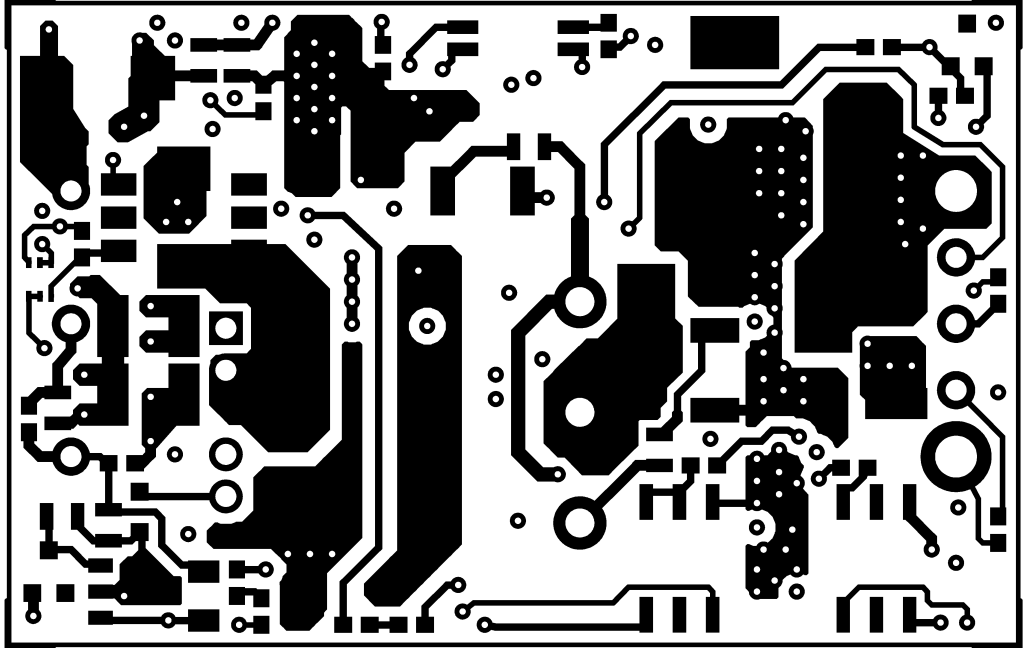

20177312


Layer 1

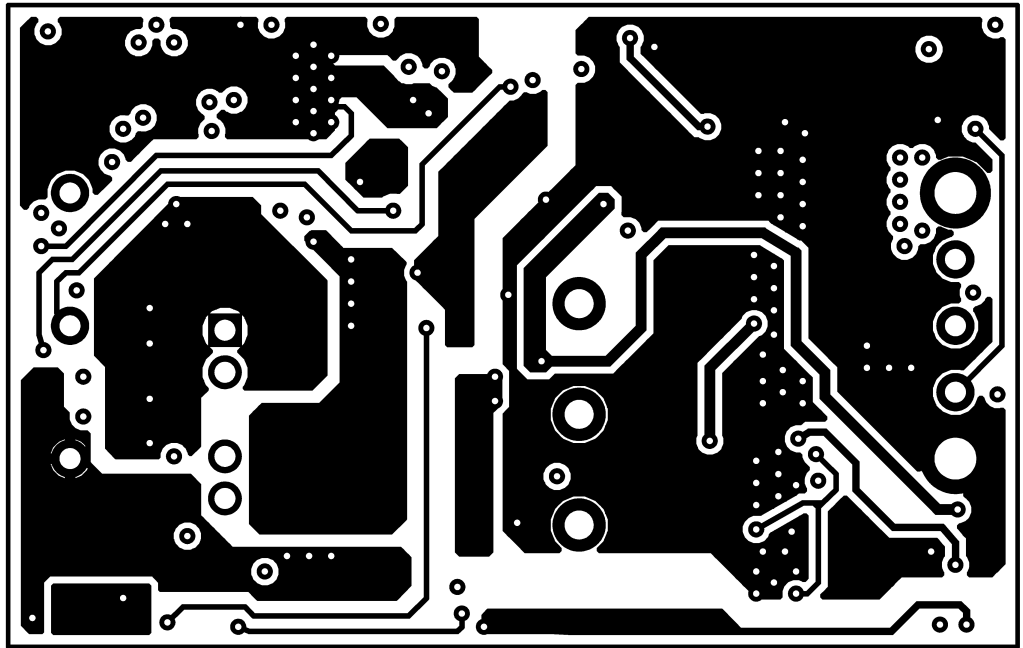

20177313


Layer 2

PCB Layouts (Continued)

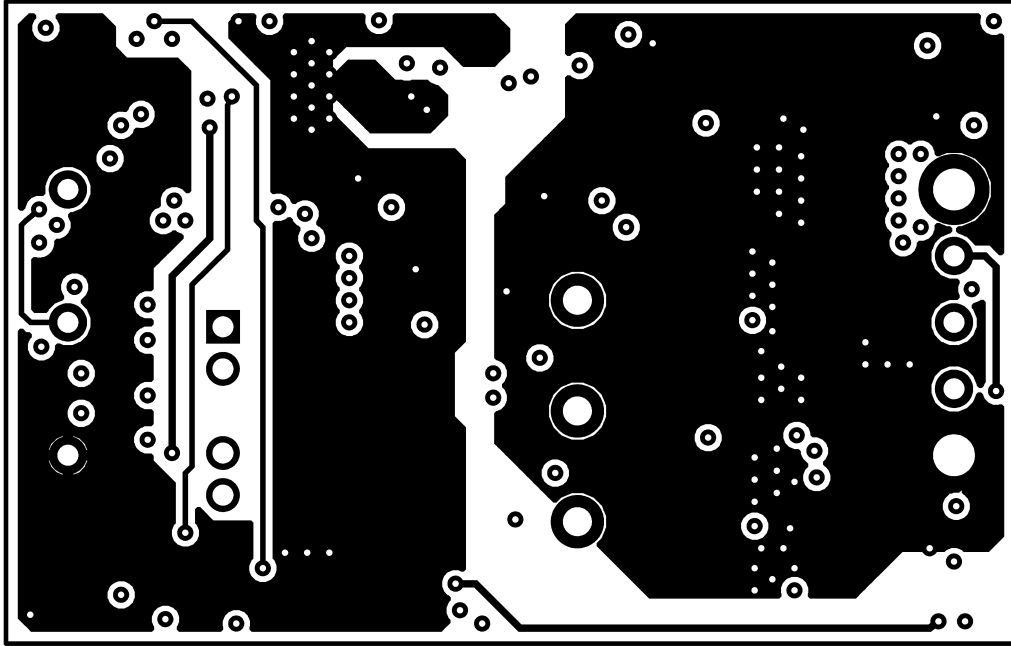

Layer 3


20177314

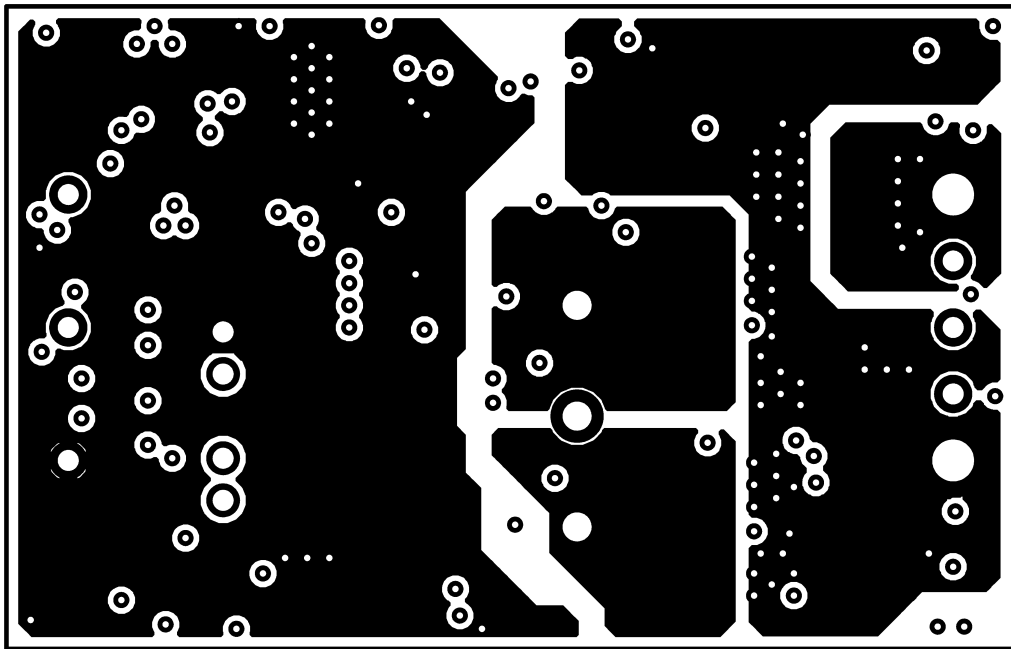

Layer 4


20177315

PCB Layouts (Continued)

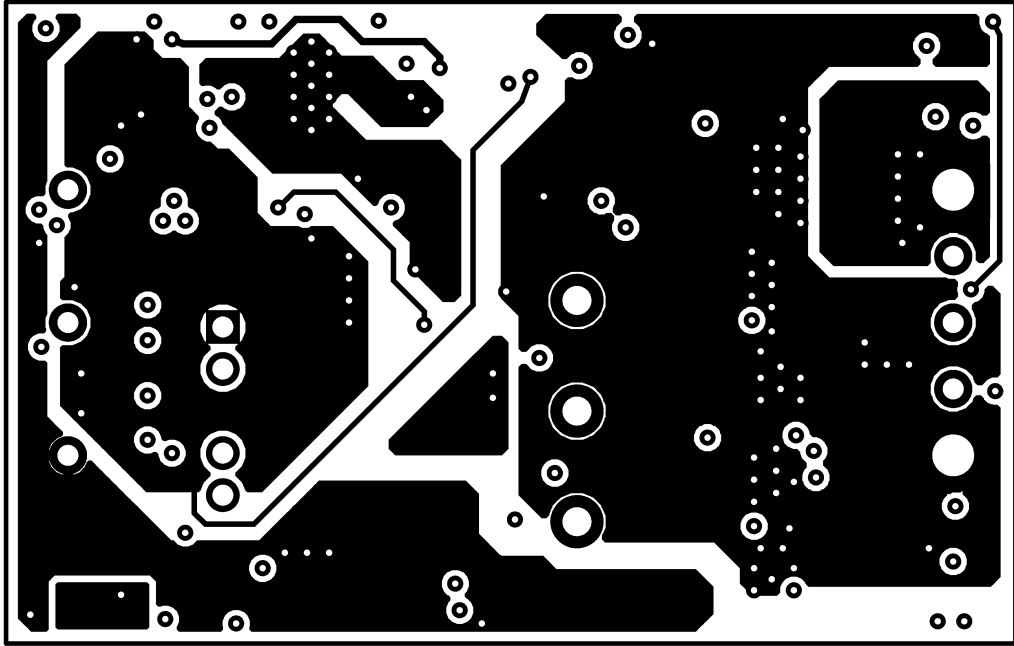

20177316

Layer 5

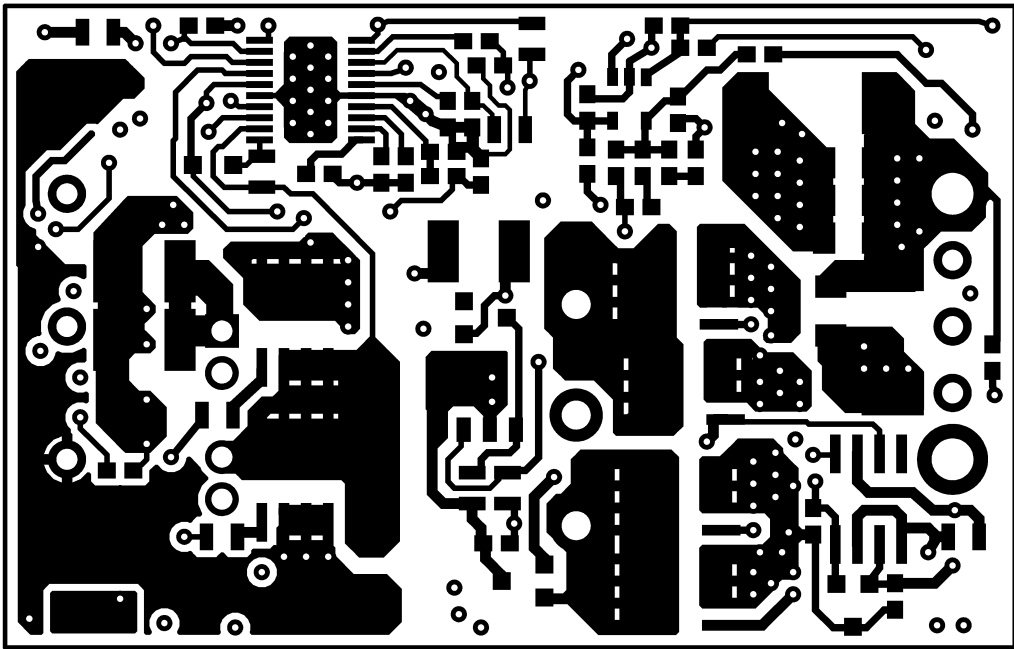

20177317

Layer 6

Notes

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor manufactures products and uses packing materials that meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.

Leadfree products are RoHS compliant.



National Semiconductor
Americas Customer
Support Center
Email: new.feedback@nsc.com
Tel: 1-800-272-9959

www.national.com

National Semiconductor
Europe Customer Support Center
Fax: +49 (0) 180-530 85 86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor
Asia Pacific Customer
Support Center
Email: ap.support@nsc.com

National Semiconductor
Japan Customer Support Center
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated