LM3670

Application Note 1348 LM3670 Evaluation Board



Literature Number: SNVA098C

LM3670 Evaluation Board

National Semiconductor Application Note 1348 Netnarin Joy Taylor October 9, 2008



Introduction

The LM3670 evaluation board is a working demonstration of a step down DC-DC converter. This application note contains information about the evaluation board. For further information on buck converter topology, device electrical characteristics, and component selection please refer to the datasheet.

General Description

The LM3670 converts high input voltages to lower output voltages with high efficiency through an inductor based switching topology. Automatic intelligent switching between PWM low-

noise and PFM low-current mode offers improved system control. LM3670 is available in both fixed output voltage options (1.2V, 1.5V, 1.6V, 1.8V, 1.875V, 2.5V, 3.3V) and adjustable voltage options range from 0.7V to 2.5V. The LM3670 is available in a SOT23-5 package.

Operating Conditions

- V_{IN} range: $2.5V \le V_{IN} \le 5.5V$
- Recommended load current: 0 mA ≤ I_{OUT} ≤ 350 mA
- Ambient temperature (T_A) range: -40C to +85C
- Junction temperature (T_{.I}) range: -40C to +125C

Typical Application

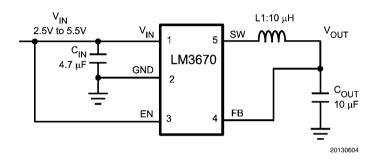


FIGURE 1. Fixed Output Voltage--Typical Application Circuit

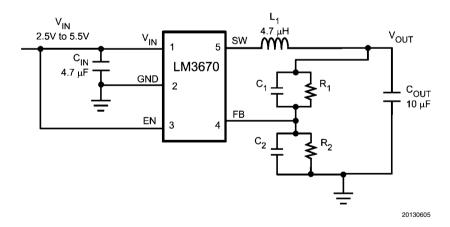


FIGURE 2. Adjustable Output Voltage—Typical Application Circuit

Output Voltage Selection for LM3670MF-ADJ

The output voltage of the adjustable parts can be programmed through the resistor network connected from V_{OUT} to V_{FB} to GND. The resistor from V_{FB} to GND (R₂) should be at least 100k Ω to keep the current sunk through this network well below 15µA quiescent current level (PFM mode with no switching) but large enough that it is not susceptible to noise. If R₂ is 200k Ω , and given the V_{FB} is 0.5V, then the current through the resistor feedback network will be 2.5µA (I_{FB} = 0.5V/R₂). The output voltage formula is:

$$V_{OUT} = V_{FB} \left(\frac{R_1}{R_2} + 1 \right)$$

V_{OUT}: output voltage (V)

V_{FB}: feedback voltage (0.5V typical)

 R_1 : feedback resistor from V_{OUT} to $V_{FB}(\Omega)$

 R_2 : feedback resistor from V_{ER} to GND (Ω)

For the fixed output voltage parts the feedback resistors are internal and R_{1} is $\Omega\Omega.$

The bypass capacitors $\mathrm{C_1}$ and $\mathrm{C_2}$ (labeled $\mathrm{C_4}$ and $\mathrm{C_5}$ on Evaluation Board) in parallel with the feedback resistors are chosen for increased stability. Below are the formulas for $\mathrm{C_1}$ and $\mathrm{C_2}$.

$$C_1 = \frac{1}{2 * \pi * R_1 * 10 \text{ kHz}}$$

$$C_2 = \frac{1}{2 * \pi * R_2 * 10 \text{ kHz}}$$

TABLE 1. Adjustable LM3670 Configurations for Various Voll

V _{OUT} (V)	$R_1(k\Omega)$	$R_2(k\Omega)$	C ₁ (pF)	C ₂ (pF)	L (µH)	C _{IN} (µF)	C _{OUT} (μF)
0.7	80.6	200	200	150	4.7	4.7	10
0.8	120	200	130	none	4.7	4.7	10
0.9	160	200	100	none	4.7	4.7	10
1.0	200	200	82	none	4.7	4.7	10
1.1	240	200	68	none	4.7	4.7	10
1.2	280	200	56	none	4.7	4.7	10
1.24	300	200	56	none	4.7	4.7	10
1.24	221	150	75	120	4.7	4.7	10
1.5	402	200	39	none	10	4.7	10
1.6	442	200	39	none	10	4.7	10
1.7	487	200	33	none	10	4.7	10
1.875	549	200	30	none	10	4.7	14.7 (10 4.7)
2.5	806	200	22	82	10	4.7	22

Powering the LM3670 for Bench Measurements

When powering the LM3670 with a bench power supply, it is recommended to place a $100\mu F$ tantalum capacitor across the V_{IN} and GND supply terminals of the bench power supply. This capacitor will reduce the input spike caused by the power

supply and long power cables. The combination of the power supply and inductance within the power cables produce a large voltage spike that may damage the device. In addition, consideration must also be looked at the enable pin of the device. The enable should never be taken high, until minimum guaranteed operating voltage of 2.7V is reached. The enable pin should also never exceed the input voltage.

Connection Diagram and Package Mark Information

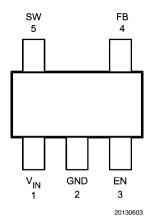



FIGURE 3. SOT23-5 Package-Top View

Pin Descriptions

Pin #	Name	Description			
1	V _{IN}	Power supply input. Connect to the input filter capacitor			
2	GND	Ground pin			
3	EN	Enable input			
4	FB	Feedback analog input. Connect to the output filter capacitor			
5	SW	Switching node connection to the internal PFET switch and NFET synchronous rectifier. Connect to an inductor with a saturation current rating that exceeds the 750 mA max. Switch Peak Current Limit Specification.			


3 www.national.com

Evaluation Board Layout

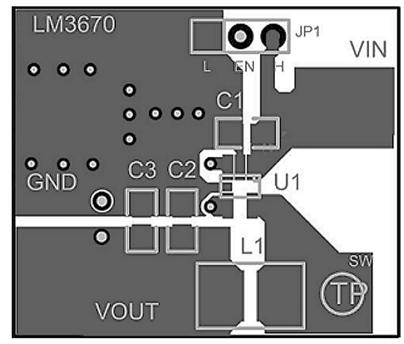

20130608

FIGURE 4. Top Layer

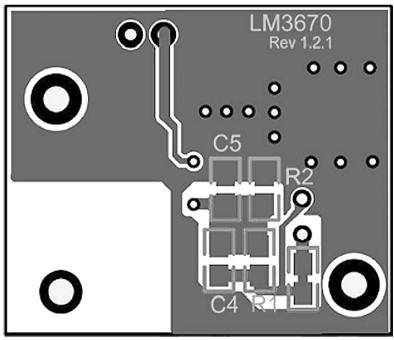

20130609

FIGURE 5. Bottom Layer

BOM For Common Configurations

	Manufacture	Manufacture #	Description	
LM3670 - 1.8V & 3.3V FIXE	D	•		
C1 (input C)	Taiyo Yuden	LMK316BJ475ML	4.7μF,10V,20%,1206	
C3 (output C)	TDK	3216X5R0J106M	10μF,6.3V,20%,1206	
C2 (aux output C)				
L1 (inductor)	Coilcraft	DO1608C-103	10μH inductor, 1.1A sat	
R1 (V _{OUT} to V _{FB})	Vishay	CRCW08050R00F	0Ω, 0805	
C4 (V _{OUT} to V _{FB})				
R2 (V _{FB} to GND)				
C5 (V _{FB} to GND)				
LM3670 - 1.2V ADJUSTAE	BLE	•	•	
C1 (input C)	Taiyo Yuden	LMK316BJ475ML	4.7 μF,10V,20%,1206	
C3 (output C)	TDK	3216X5R0J106M	10 μF,6.3V,20%,1206	
C2 (aux output C)				
L1 (inductor)	Coilcraft	DO1608C-472	4.7 µH inductor, 1.5A sat	
R1 (V _{OUT} to V _{FB})	Vishay	CRCW08052803F	280 kΩ, 0805, 1%	
C4 (V _{OUT} to V _{FB})	Vishay	VJ0805Y560KXXA	56 pF, 0805, 10%	
R2 (V _{FB} to GND)	Vishay	CRCW08052003F	200 kΩ, 0805, 1%	
C5 (V _{FB} to GND)				
LM3670 - 1.5V ADJUSTAE	BLE	•		
C1 (input C)	Taiyo Yuden	LMK316BJ475ML	4.7 μF,10V,20%,1206	
C3 (output C)	TDK	3216X5R0J106M	10 μF,6.3V,20%,1206	
C2 (aux output C)				
L1 (inductor)	Coilcraft	DO1608C-103	10 μH inductor, 1.1A sat	
R1 (V _{OUT} to V _{FB})	Vishay	CRCW08054023F	402 kΩ, 0805, 1%	
C4 (V _{OUT} to V _{FB})	Vishay	VJ0805A390KXAA	39 pF, 0805, 10%	
R2 (V _{FB} to GND)	Vishay	CRCW08052003F	200 kΩ, 0805, 1%	
C5 (V _{FB} to GND)				
LM3670 - 2.5V ADJUSTAE	BLE			
C1 (input C)	Taiyo Yuden	LMK316BJ475ML	4.7 μF,10V,20%,0805	
C3 (output C)	Taiyo Yuden	JMK316BJ226ML	22 μF,6.3V,20%, 1206	
C2 (aux output C)				
L1 (inductor)	Coilcraft	DO1608C-103	10 μH inductor, 1.1A sat	
R1 (V _{OUT} to V _{FB})	Vishay	CRCW08058063F	806 kΩ, 0805, 1%	
C4 (V _{OUT} to V _{FB})	Vishay	VJ0805A220KXAA	22 pF, 0805, 10%	
R2 (V _{FB} to GND)	Vishay	CRCW08052003F	200 kΩ, 0805, 1%	
C5 (V _{FB} to GND)	Vishay	VJ0805A820KXAA	82 pF, 0805, 10%	
COMMON TO ALL		•		
V _{IN} banana jack - red	Johnson Components	108-0902-001	connector, insulated banana jack (red)	
V _{OUT} banana jack - yellow	Johnson	108-0907-001	connector, insulated banana jack (yellow)	
	Components			
GND banana jack - black	Johnson Components	108-0903-001	connector, insulated banana jack (black)	

www.national.com

Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Pr	oducts	Design Support		
Amplifiers	www.national.com/amplifiers	WEBENCH	www.national.com/webench	
Audio	www.national.com/audio	Analog University	www.national.com/AU	
Clock Conditioners	www.national.com/timing	App Notes	www.national.com/appnotes	
Data Converters	www.national.com/adc	Distributors	www.national.com/contacts	
Displays	www.national.com/displays	Green Compliance	www.national.com/quality/green	
Ethernet	www.national.com/ethernet	Packaging	www.national.com/packaging	
Interface	www.national.com/interface	Quality and Reliability	www.national.com/quality	
LVDS	www.national.com/lvds	Reference Designs	www.national.com/refdesigns	
Power Management	www.national.com/power	Feedback	www.national.com/feedback	
Switching Regulators	www.national.com/switchers			
LDOs	www.national.com/ldo			
LED Lighting	www.national.com/led			
PowerWise	www.national.com/powerwise			
Serial Digital Interface (SDI)	www.national.com/sdi			
Temperature Sensors	www.national.com/tempsensors			
Wireless (PLL/VCO)	www.national.com/wireless			

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2008 National Semiconductor Corporation

For the most current product information visit us at www.national.com



National Semiconductor Americas Technical Support Center Email: support@nsc.com Tel: 1-800-272-9959 National Semiconductor Europe Technical Support Center Email: europe.support@nsc.com German Tel: +49 (0) 180 5010 771 English Tel: +44 (0) 870 850 4288 National Semiconductor Asia Pacific Technical Support Center Email: ap.support@nsc.com

National Semiconductor Japan Technical Support Center Email: jpn.feedback@nsc.com

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products Applications

Audio www.ti.com/audio Communications and Telecom www.ti.com/communications **Amplifiers** amplifier.ti.com Computers and Peripherals www.ti.com/computers dataconverter.ti.com Consumer Electronics www.ti.com/consumer-apps **Data Converters DLP® Products** www.dlp.com **Energy and Lighting** www.ti.com/energy DSP dsp.ti.com Industrial www.ti.com/industrial Clocks and Timers www.ti.com/clocks Medical www.ti.com/medical Interface interface.ti.com Security www.ti.com/security

Logic Space, Avionics and Defense <u>www.ti.com/space-avionics-defense</u>

Power Mgmt power.ti.com Transportation and Automotive www.ti.com/automotive
Microcontrollers microcontroller.ti.com Video and Imaging www.ti.com/video

RFID <u>www.ti-rfid.com</u>
OMAP Mobile Processors www.ti.com/omap

Wireless Connectivity www.ti.com/wirelessconnectivity

TI E2E Community Home Page <u>e2e.ti.com</u>